

Digital microsystems design

Marius Marcu

2020

Objectives


- Specific objectives
 - Internal architecture and external interfaces of x86 processors and their functional behavior
 - Memory connectivity

Outline

- Microprocessor bus
 - Amplifying bus lines
 - Demultiplexing bus lines
 - Decoding address lines
 - Data transfers size
- Memory decoding
- Summary

Buses

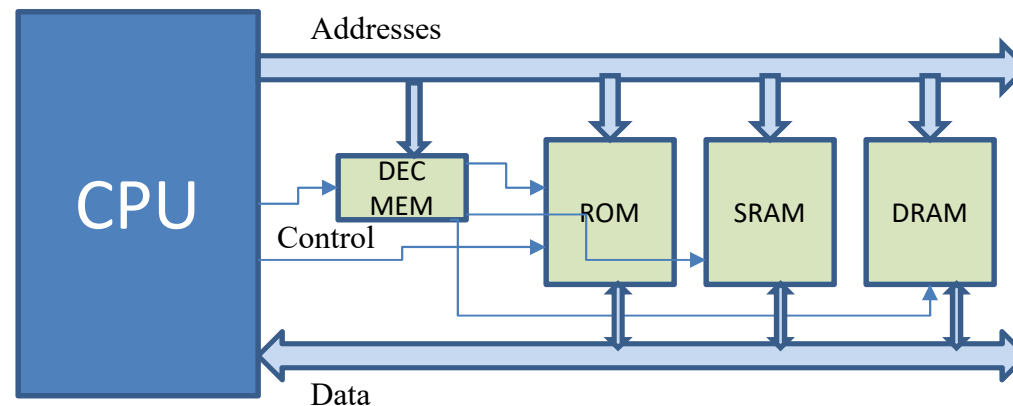- There are several aspects to be addressed when connecting memory and I/O to microprocessor buses:
 - Signal amplifying
 - Signal demultiplexing
 - Slave selection (decoding)
 - Data transfers sizes



Buses

- Amplifying bus lines
 - Fan-out of the processor
 - Example:
 - How many TTL gates the given microprocessor can drive?

Circuit type	I_{OH}	I_{OL}	I_{IH}	I_{IL}
Microprocessor	250 μA	1,8 mA	10 μA	10 μA
SRAM	1 mA	2,1 mA	2 μA	2 μA
Parallel I/O controller	400 μA	2,5 mA	10 μA	10 μA
CMOS gates	8 mA	8 mA	1 μA	1 μA
TTL gates	800 μA	16 mA	40 μA	1,6 mA


Buses

- Amplifying bus lines
 - Example:
 - 8086 processor can drive maximum one TTL gate
 - How many CMOS gates 8086 processor can drive?

Circuit type	I_{OH}	I_{OL}	I_{IH}	I_{IL}
Microprocessor	250 μA	1,8 mA	10 μA	10 μA
SRAM	1 mA	2,1 mA	2 μA	2 μA
Parallel I/O controller	400 μA	2,5 mA	10 μA	10 μA
CMOS gates	8 mA	8 mA	1 μA	1 μA
TTL gates	800 μA	16 mA	40 μA	1,6 mA



Buses

- Amplifying output lines:

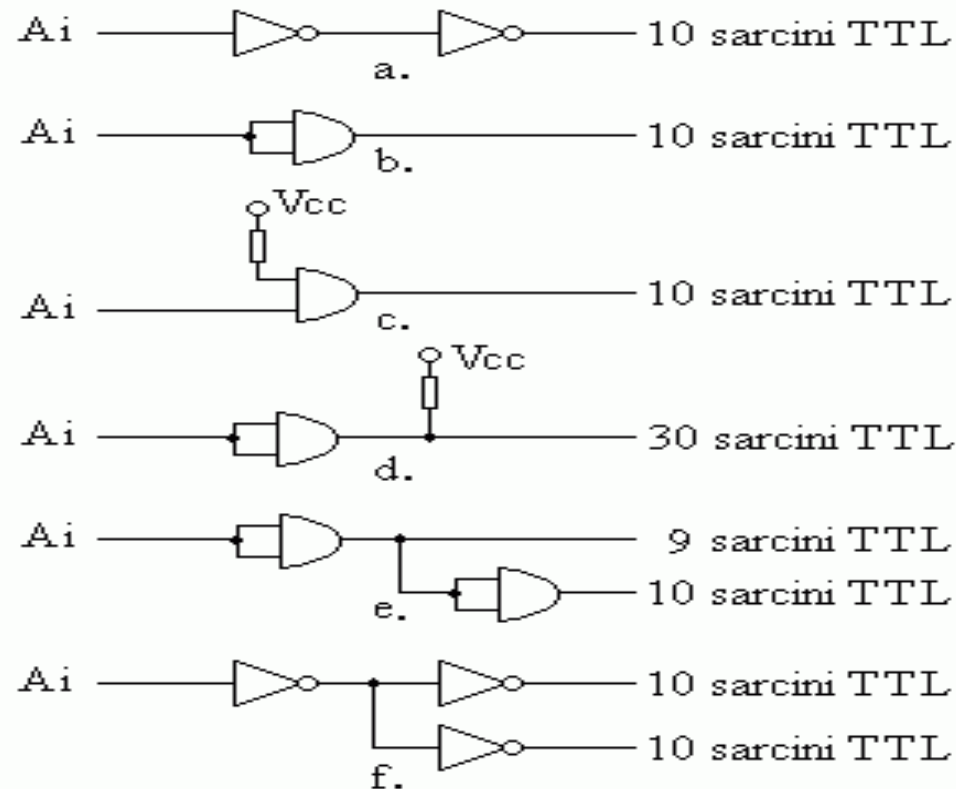



Buses

- Amplifying tristate lines

  


Buses

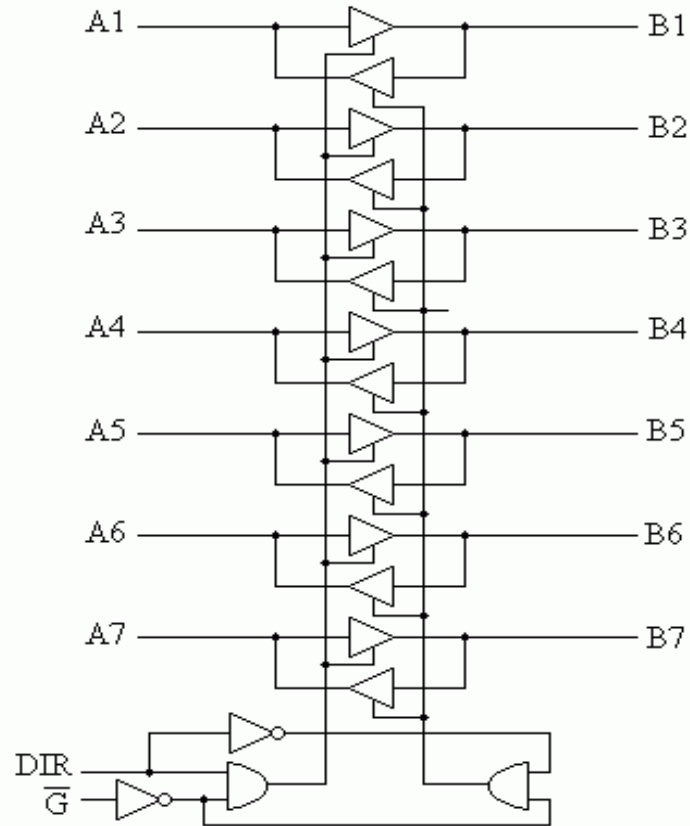 - Amplifying bidirectional lines:
 - 74LS245




Buses

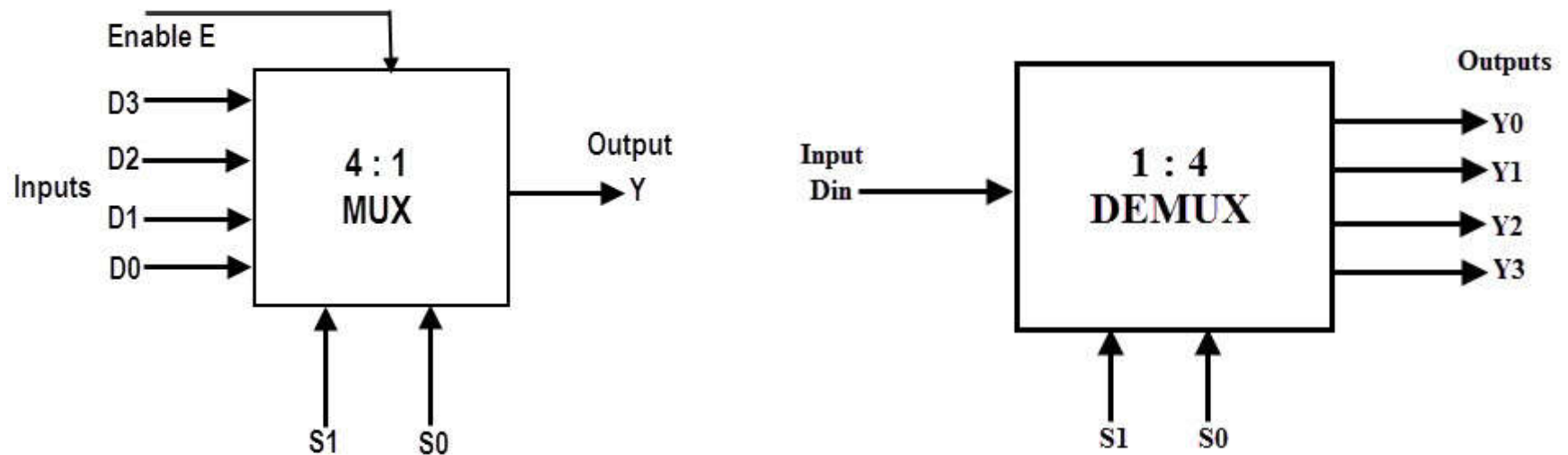- Demultiplexing time multiplexed bus lines
 - Time multiplexed signals




Buses

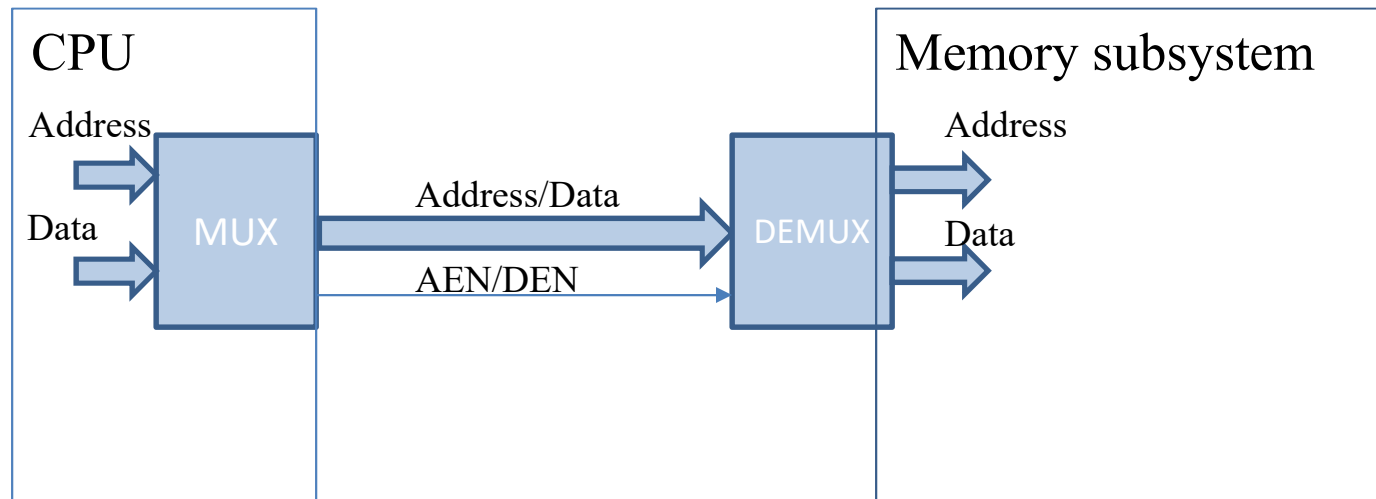- Demultiplexing time multiplexed bus lines
 - Time multiplexed address and data values – reduce the number of CPU pins
 - Bus slaves (memories, I/O ports) require address values to be stable during the whole access cycle




Buses

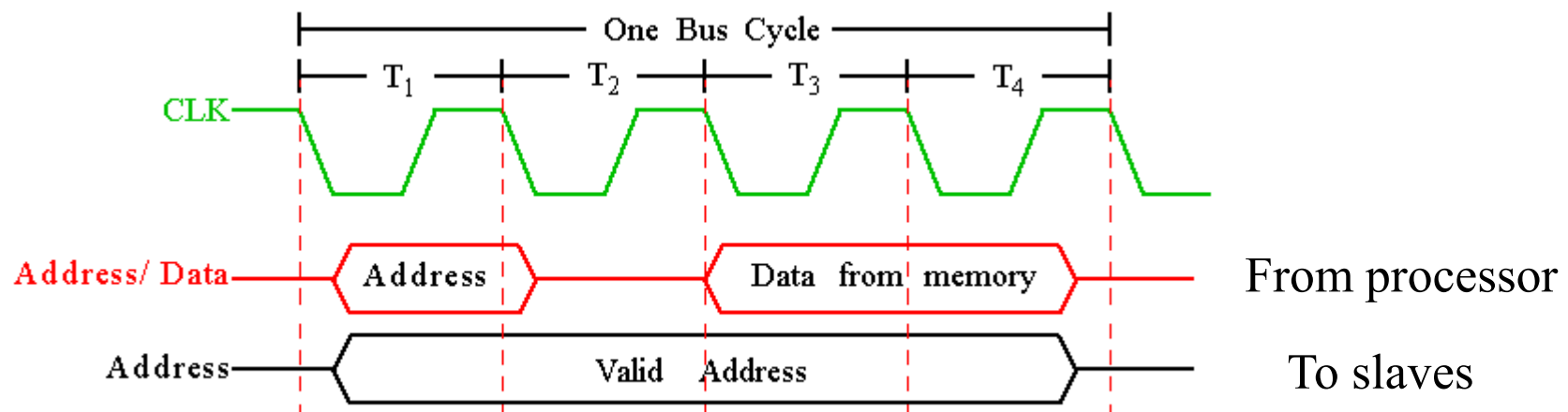- Demultiplexing time multiplexed bus lines
 - Some processors multiplex address and data lines
 - The address is sent first followed by data time slot (RD/WR)
 - Memories need the address for the whole cycle
 - How demultiplexing addresses/data lines can be implemented?




Buses

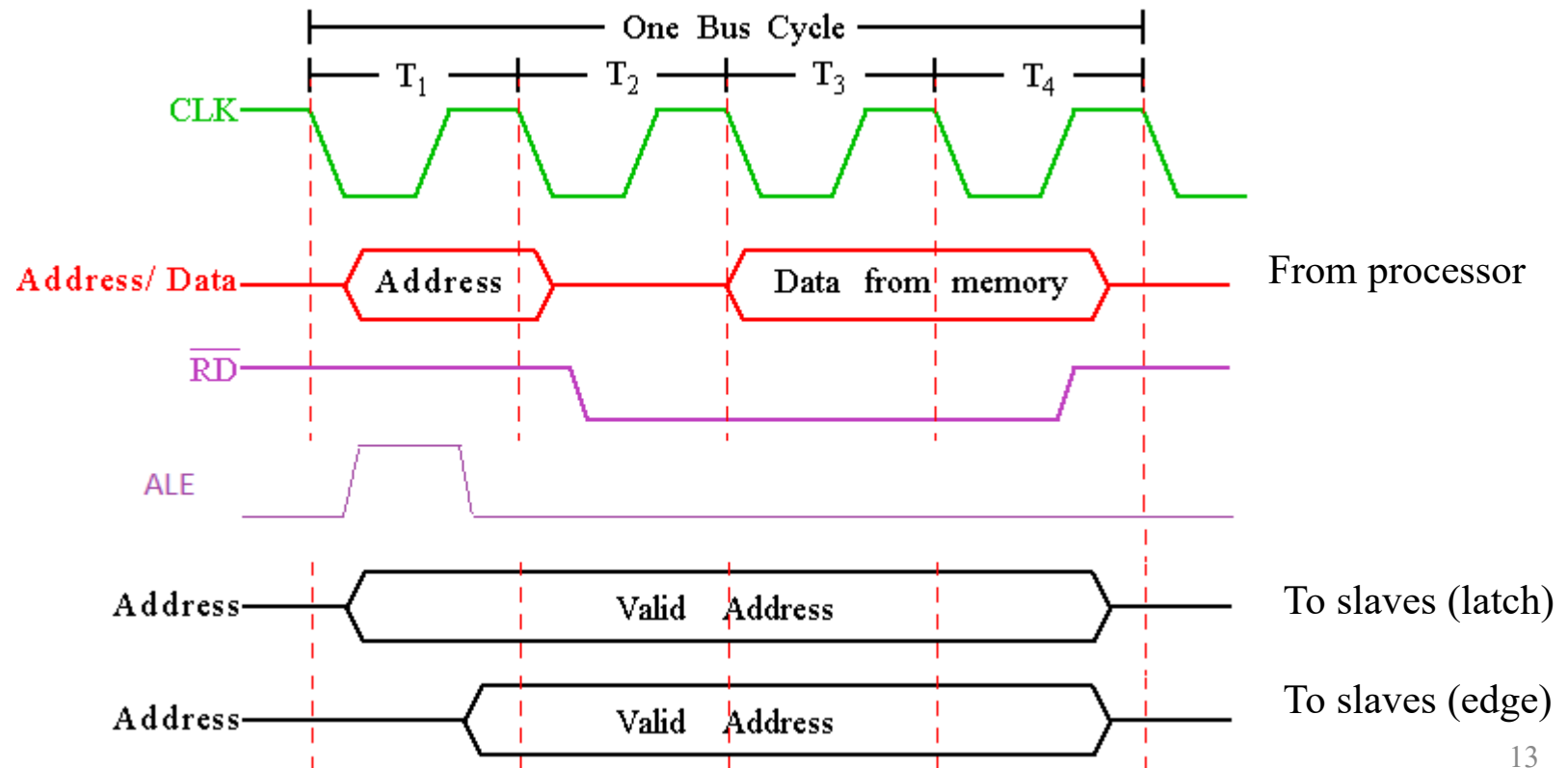- Demultiplexing
 - Address latch enable – latches the address into the address buffers for demultiplexing





Buses

- Demultiplexing

 


Buses

 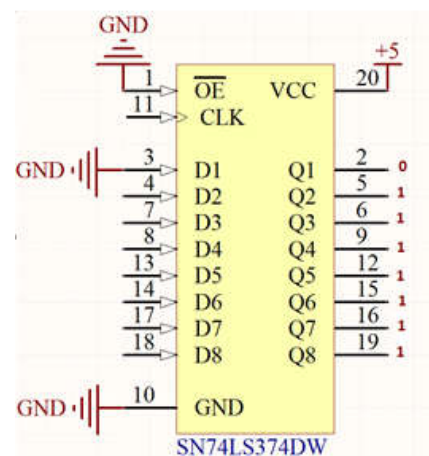- Demultiplexing address and data values
 - Using latches/registers to store the address while the processor transfers data to/from bus slaves (bus cycles)
 - 74x373 (level), 74x374 (edge)




Buses

- Central demultiplexing
 - Centralized

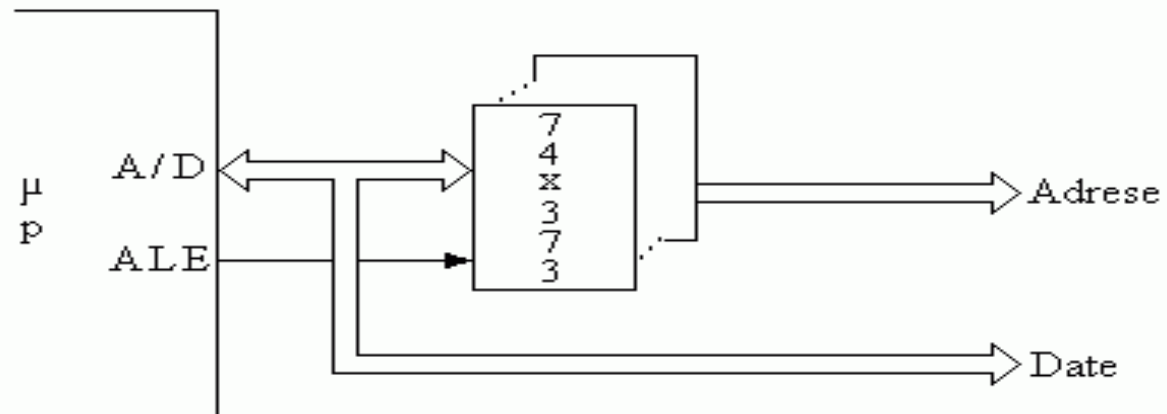

Buses

- Local demultiplexing
 - Distributed

 


Buses

- Decoding
 - Master – slave transfers
 - One active master and one selected slave
 - Generates selection signals for each slave module in the system (memory and I/O) implementing the memory/I/O map
 - Memory address space
 - Memory decoder
 - I/O address space
 - I/O decoder


Buses

- Central decoding
 - Centralized

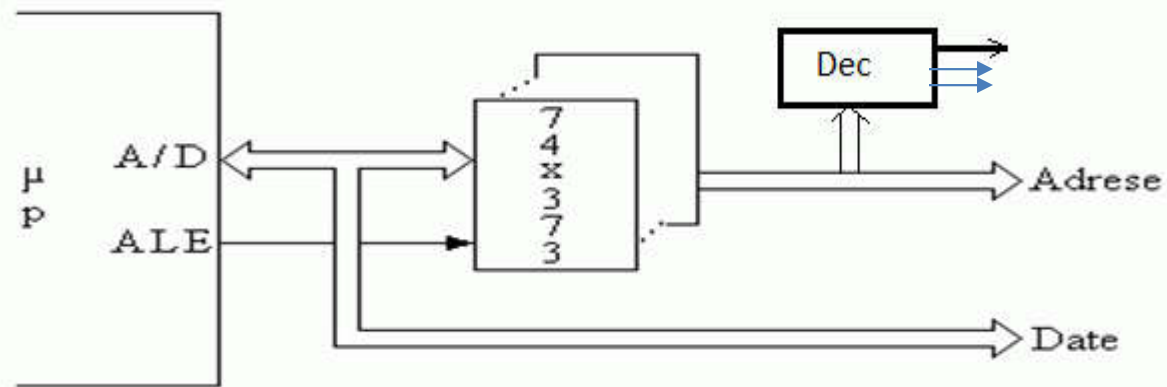

Buses

- Local decoding
 - Distributed

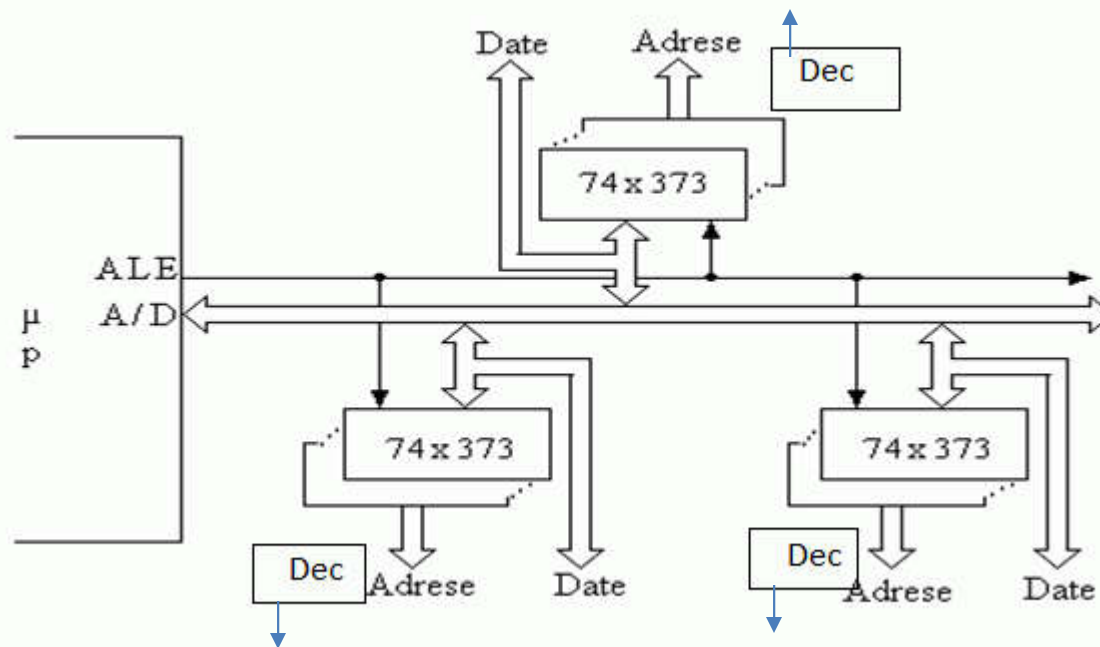


Buses

- Decoding
 - Decoding circuits
 - 74x138: decoder 3 \rightarrow 8,
 - 74x139: decoder 2 x 2 \rightarrow 4,
 - 74x42: decoder 4 \rightarrow 10,
 - 74x154: decoder 4 \rightarrow 16.

Buses


- 74x138

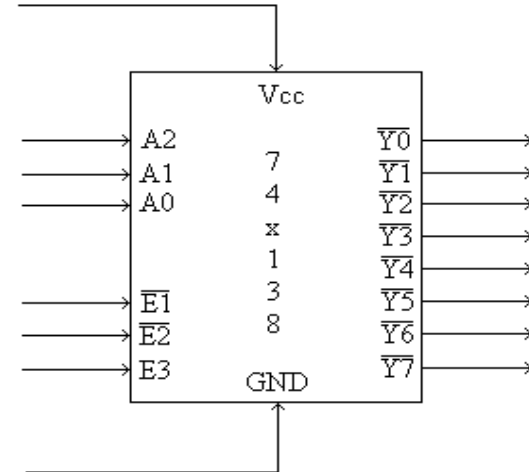

E3	/E2	/E1	A2	A1	A0	/Y7	/Y6	/Y5	/Y4	/Y3	/Y2	/Y1	/Y0
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1
0	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	1	X	X	X	1	1	1	1	1	1	1	1

Buses


- 74x139

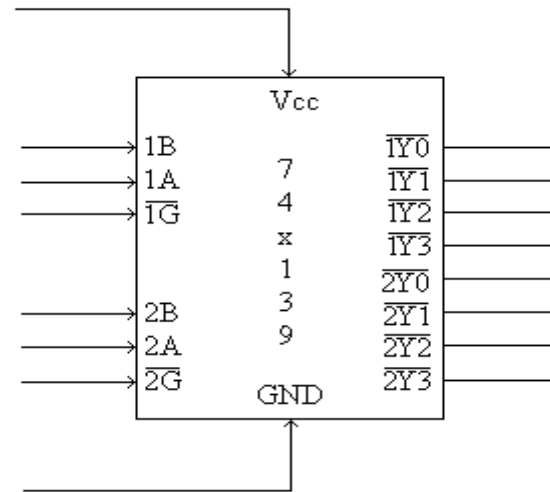

/iG	iB	iA	/iY3	/iY2	/iY1	/iY0
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	X	X	1	1	1	1

Memory decoder

- Memory map
 - x86/x64

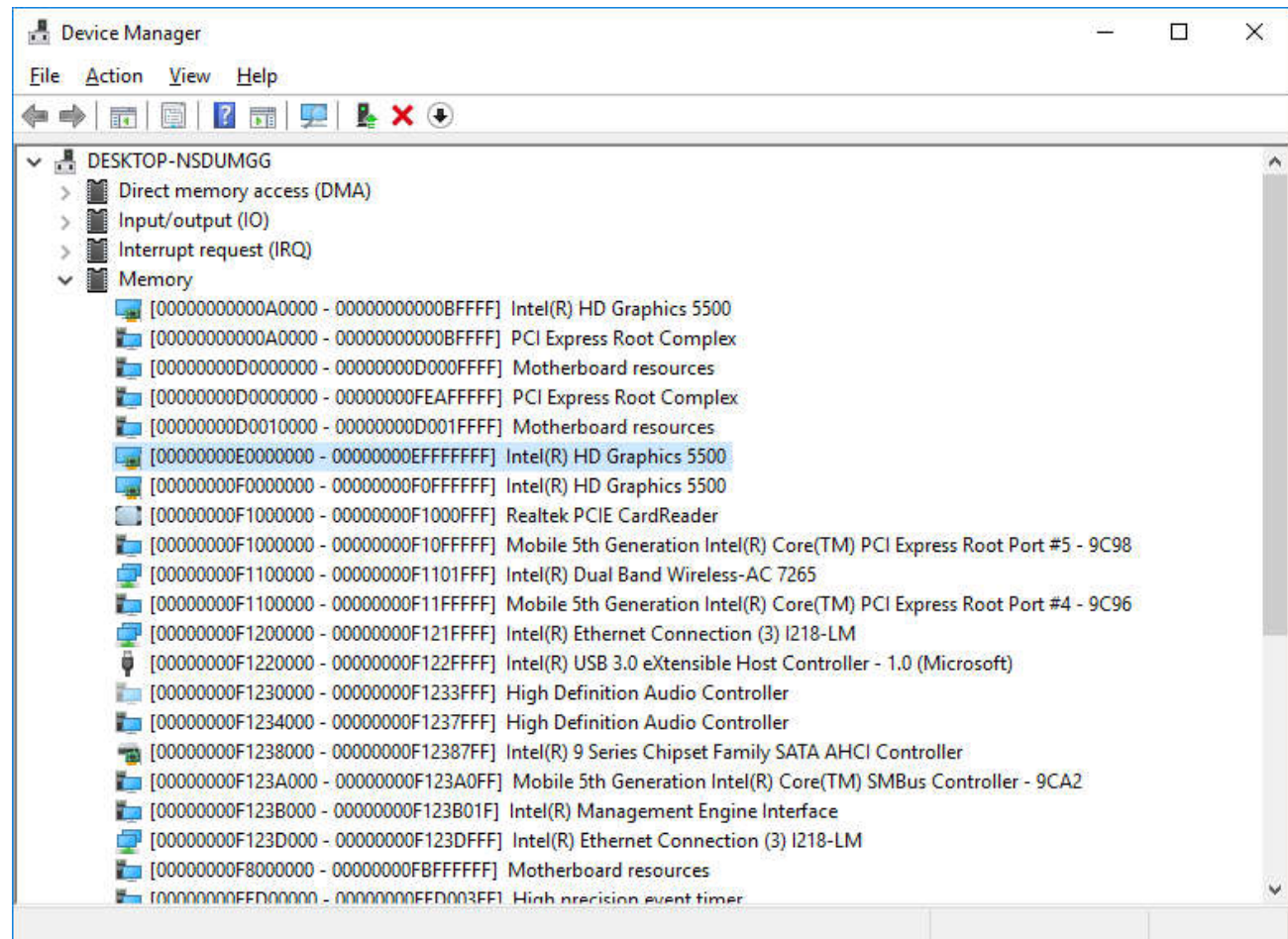

Memory decoder

Address Map for processor ps7_cortexa9_[0-1]

- Memory map
 - ARM

Cell	Base Addr	High Addr	Slave I/f	Mem/Reg
ps7_intc_dist_0	0xf8f01000	0xf8f01fff		REGISTER
ps7_gpio_0	0xe000a000	0xe000afff		REGISTER
ps7_scutimer_0	0xf8f00600	0xf8f006ff		REGISTER
tree_proc_axi_0	0x40000000	0x400fffff	S_AXI_F	REGISTER
tree_proc_axi_0	0x41000000	0x410fffff	S_AXI_C	REGISTER
ps7_slcr_0	0xf8000000	0xf8000fff		REGISTER
ps7_scuwdt_0	0xf8f00620	0xf8f006ff		REGISTER
ps7_l2cachec_0	0xf8f02000	0xf8f02fff		REGISTER
ps7_scuc_0	0xf8f00000	0xf8f000fc		REGISTER
ps7_qspi_linear_0	0xfc000000	0xfcffffff		FLASH
ps7_pmu_0	0xf8893000	0xf8893fff		REGISTER
ps7_afi_1	0xf8009000	0xf8009fff		REGISTER
ps7_afi_0	0xf8008000	0xf8008fff		REGISTER
ps7_qspi_0	0xe000d000	0xe000dfff		REGISTER
ps7_usb_0	0xe0002000	0xe0002fff		REGISTER
ps7_afi_3	0xf800b000	0xf800bfff		REGISTER
ps7_afi_2	0xf800a000	0xf800afff		REGISTER
ps7_globaltimer_0	0xf8f00200	0xf8f002ff		REGISTER
ps7_dma_s	0xf8003000	0xf8003fff		REGISTER
ps7_iop_bus_config_0	0xe0200000	0xe0200fff		REGISTER
ps7_xadc_0	0xf8007100	0xf8007120		REGISTER
ps7_ddr_0	0x00100000	0x3fffffff		MEMORY
ps7_ddrc_0	0xf8006000	0xf8006fff		REGISTER
ps7_ocmc_0	0xf800c000	0xf800cfff		REGISTER
ps7_pl310_0	0xf8f02000	0xf8f02fff		REGISTER
ps7_uart_1	0xe0001000	0xe0001fff		REGISTER
ps7_coresight_comp_0	0xf8800000	0xf88fffff		REGISTER
ps7_i2c_0	0xe0004000	0xe0004fff		REGISTER
ps7_ttc_0	0xf8001000	0xf8001fff		REGISTER
ps7_scugic_0	0xf8f00100	0xf8f001ff		REGISTER
ps7_ethernet_0	0xe000b000	0xe000bfff		REGISTER
ps7_dev_cfg_0	0xf8007000	0xf80070ff		REGISTER
ps7_dma_ns	0xf8004000	0xf8004fff		REGISTER
ps7_sd_0	0xe0100000	0xe0100fff		REGISTER
ps7_gpv_0	0xf8900000	0xf89fffff		REGISTER
ps7_ram_1	0xffff0000	0xffffdfff		MEMORY
ps7_ram_0	0x00000000	0x0002ffff		MEMORY

Memory decoder

- Memory map - example
 - Memory size = ending address - starting address + 1
 - 0xE0000000-0xFFFFFFFF
 - $0x0FFFFFFF + 1 = 2^{28}B = 2^8 \cdot 2^{20}B = 256\text{ MB}$
 - 0x40000000-0x400FFFFFFF
 - $0x000FFFFFFF + 1 = 1\text{MB}$
 - 0x00000000-0x0002FFFFF
 - $0x2FFFFF + 1 = 0x30000 = 2^{17} + 2^{16} = 128\text{KB} + 64\text{KB} = 192\text{KB}$
 - 0x00000000-0x3FFFFFFF
 - $0x3FFFFFFF + 1 = 2^{30}B = 1\text{GB}$

Memory decoder

- Component of a digital system that generates selection signal for the slave module addressed by in the current bus transaction
- Also known as address decoder
- Inputs: most significant bits of the address bus
- Outputs: selection signals for each memory module
- Design steps
 - Memory requirements and constraints
 - Memory setup
 - Memory map
 - Logic design
 - Optimization (speed, space, complexity)

Memory decoder

- Memory requirements and constraints
 - Processor requirements and constraints:
 - Reset address – covered by ROM memory
 - Interrupts vectors table – RAM memory
 - Address space – max memory size
 - Data bus width / data transfer sizes
 - Memory circuits to use:
 - Memory type, memory size
 - Data pins
 - Operating system requirements
 - OS kernel code and data
 - Compiler and applications
 - Linker setup
 - code, stack, data, heap,...

Memory decoder

- Memory setup
 - Memory circuits parameters:
 - Size (number of memory locations to store)
 - Type (ROM, SRAM, DRAM)
 - Number of address lines (n): size = 2^n
 - Number of data lines
 - number of circuits needed in one block to satisfy uP bus data width requirements
 - Addresses range: 0 - 2^n-1 (hexadecimal)

Memory decoder

- Memory setup
 - Number of circuits
 - Size of required memory / Size of available circuits
 - Take care of measurement units / data width
 - Number of blocks
 - Number of circuits needed in one block to satisfy uP bus data width requirements
 - Number of circuits per block = $\text{uP data bus width} / \text{memory data bus width}$
 - Address space requirements for each memory block

Memory decoder

- Memory setup
 - Example
 - Example – connect 1MB of memory using 256 KB memory circuits to a 16 bits data bus processor
 - How many circuits are needed?
 - How are they connected to the processor?
 - How many blocks are obtained?
 - What is the address space required by each block?

Memory decoder

- Memory setup example
 - Number of circuits = $1\text{MB} / 256\text{ KB} = 4$ circuits
 - Number of circuits per block = $16\text{ bits} / 8\text{ bits} = 2$ circuits
 - Number of blocks = $4 / 2 = 2$
 - Each block has $2 \times 256\text{ KB} = 512\text{ KB} = 2^{19}\text{B}$
 - `0x00000000-0x0007FFFF`

Memory decoder


- Memory setup
 - Example
 - Example – connect 1MB of memory using 256 Kx16bits memory circuits to a 16 bits data bus processor
 - How many circuits are needed?
 - How are they connected to the processor?
 - How many blocks are obtained?
 - What is the address space required by each block?

Memory decoder

- Memory setup example
 - Number of circuits = $1\text{MB} / 256 \text{ K} \times 16\text{bits} = 1 \text{ MB} / 512\text{KB} = 2$ circuits
 - Number of circuits per block = $16 \text{ bits} / 16 \text{ bits} = 1$ circuit
 - Number of blocks = $2 / 1 = 2$
 - Each block has $2 \times 256 \text{ KB} = 512 \text{ KB} = 2^{19}\text{B}$
 - `0x00000000-0x0007FFFF`

Memory decoder

 - Logic design
 - Most significant address bits are used to select slave blocks
 - What happens when using 1 bit (MSbit) to select memory blocks?
 - Two blocks to select
 - Example:
 - 1 MB address space
 - 20 address lines
 - A19 memory block selection
 - A18-0 memory location selection
 - B1: 00000 – 7FFFFH (512 kB)
 - B2: 80000H – FFFFFH (512 kB)



Memory decoder

- Linear decoding
 - Ad-hoc logic design
 - 1 bit – 2 blocks of the same size
 - 2 bits – 4 blocks of the same size
 - ...
 - Simple design
 - Less circuits
 - Lower resolution
 - Not efficient for small circuits or various sizes

Memory decoder

- Linear decoding
 - Example:
 - 1 MB address space
 - A19-0 address lines
 - 20 address lines
 - A19,A18 memory block selection
 - A17-0 memory location selection
 - Memory map
 - B1: 00000 – 3FFFFH (256 kB)
 - B2: 40000 – 7FFFFH (256 kB)
 - B3: 80000 – BFFFFH (256 kB)
 - B2: C0000H – FFFFFH (256 kB)

A19	A18	Decoder
0	0	B1
0	1	B2
1	0	B3
1	1	B4

Memory decoder

- Logic design and implementation
 - Methods
 - Linear decoding
 - Complete decoding
 - Incomplete decoding
- Optimization
 - Complexity
 - Speed
 - Circuits
 - Address range

Memory decoder

- Memory map – design rules
 - Apply application's requirements and constraints
 - High memory requirements – memories will fill all processor's address space – complete decoding
 - Low memory requirements – partial coverage of processor's address space – incomplete decoding
 - For every memory block an address range within the processor's address space has to be allocated
 - (1) Every memory circuit will receive at least an address range within processor's address space
 - (2) Address ranges allocated to any two different blocks should not overlap each other
 - (3) Starting address allocated to a memory block should be multiple of its size
 - $\text{starting_block_address} = k \times \text{block_size}$

Memory decoder

- Memory map – design steps
 - Establish the memory setup (based on the requirements and the available circuits)
 - Number of circuits
 - Number of blocks
 - Size of blocks and address space
 - Design the memory map using the design rules
 - Start with the address space requirements
 - Select an address range for each memory block in the uP address space

Memory decoder

- Memory map – design example
 - Design the memory map for the following memory requirements of a 16 bits uP
 - Memory type ROM: 128 KB using 64Kx16 bits circuits
 - Memory type RAM: 128 KB using 32Kx8 bits circuits

Memory decoder

- Memory map – design example
 - ROM:
 - Number of circuits: 1
 - Number of blocks: 1
 - Size of block: 128KB
 - Address space: 0x00000-0x1FFFF
 - RAM:
 - Number of circuits: 4
 - Number of blocks: 2
 - Size of block: 64KB
 - Address space: 0x00000-0x0FFFF

Memory decoder

- Memory map – design example
 - ROM: 0x00000 – 0x1FFFF
 - RAM1: 0x40000 – 0x4FFFF
 - RAM2: 0x50000 – 0x5FFFF

Memory decoder

- Complete decoding
 - All address lines of the processor are used by memory decoder and memory circuits
 - MSbits connected to decoder
 - LSbits connected to memories
 - LSbits selection at block level (A0 – 16 bits)
 - Decoding table
 - Columns: address lines
 - Rows: 2 lines for each memory block
 - starting address and ending address allocated for that block in the memory map

Memory decoder

- Complete decoding
 - Example – design the memory decoder for the following memory map of a 16 bits processor:
 - 00000H – 1FFFFH – memory block B1, 64K x 16 bits,
 - 40000H – 4FFFFH – memory block B2, 2x32K x 8 bits,
 - 50000H – 5FFFFH – memory block B3, 2x32K x 8 bits.

Memory decoder

- Decoding table

A 19	A 18	A 17	A 16	A 15	A 14	A 13	A 12	A 11	A 10	A9	A8	A7	A6	A5	A4	A3	A2	A1	M E M
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	B1
0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	B2
0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	B3
0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	

Memory decoder

- Decoding table


A 19	A 18	A 17	A 16	A 15	A 14	A 13	A 12	A 11	A 10	A9	A8	A7	A6	A5	A4	A3	A2	A1	M E M
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	B1
0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	B2
0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	B3
0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	

Memory decoder

- Complete decoding
 - For every memory block, we select columns starting with MSb, having the same logic value of both starting address and ending address
 - The selection function of every memory block can be computed based on the logic values of the most significant bits of address bus
 - The selection function uniquely identifies the memory block it is computed for

Memory decoder

 - Decoding (selection) functions
 - $SEL_{C1} = \overline{A19} * \overline{A18} * \overline{A17}$
 - $SEL_{C2} = \overline{A19} * A18 * \overline{A17} * \overline{A16}$
 - $SEL_{C3} = \overline{A19} * A18 * \overline{A17} * A16$
- Decoder implementation




Memory decoder

- Selection signals are active on 0 logic

$$- /SEL_{C1} = \overline{A19} * \overline{A18} * \overline{A17}$$

$$- /SEL_{C2} = \overline{A19} * A18 * \overline{A17} * \overline{A16}$$

 
$$- /SEL_{C3} = \overline{A19} * A18 * \overline{A17} * A16$$



Memory decoder

- Convention to represent inverse logic

 - $\overline{\text{SEL}}_{C1} = \overline{A19} * \overline{A18} * \overline{A17}$
- $\overline{\text{SEL}}_{C2} = \overline{A19} * A18 * \overline{A17} * \overline{A16}$
- $\overline{\text{SEL}}_{C3} = \overline{A19} * A18 * \overline{A17} * A16$



Memory decoder

- Complete decoding
 - Example – design the memory decoder for the following memory map:
 - 00000H – 1FFFFH – memory type ROM, 64K x 16 bits, using memory circuits of 32 KB
 - 40000H – 4FFFFH – memory type SRAM, 32K x 16 bits, using memory circuits of 16 KB
 - 80000H – 9FFFFH – memory type DRAM, 32K x 16 bits, using memory circuits of 32K x 1 bit

Memory decoder

- Incomplete decoding
 - Incomplete decoding is similar to complete decoding, but it does not use all lines of processor's address bus
 - We start with decoding table, trying to identify columns with the same logical value for every memory block
 - These address lines do not impact selection of any memory block
 - These lines can be skipped by decoder in order to simplify its implementation

Memory decoder

- Incomplete decoding
 - The consequence of using less address lines for decoding is an inefficient usage of processor address space
 - If we omit one address line when generating selection function for one memory block, that block will have two address ranges within processor's address space
 - If we omit two address lines, the memory block will occupy four address ranges

Memory decoder

- Incomplete decoding
 - Example – design the memory decoder for the following memory map:
 - 00000H – 0FFFFH – memory circuit C1, 32K x 16 bits,
 - 40000H – 4FFFFH – memory circuit C2, 32K x 16 bits,
 - 80000H – 8FFFFH – memory circuit C3, 32K x 16 bits,
 - C0000H – CFFFFH – memory circuit C4, 32K x 16 bits.

Memory decoder

- Incomplete decoding

A 19	A 18	A 17	A 16	A 15	A 14	A 13	A 12	A 11	A 10	A9	A8	A7	A6	A5	A4	A3	A2	A1	C
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 1
0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 2
0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 3
1	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 4
1	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	

Memory decoder

- Incomplete decoding

A 19	A 18	A 17	A 16	A 15	A 14	A 13	A 12	A 11	A 10	A9	A8	A7	A6	A5	A4	A3	A2	A1	C
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 1
0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 2
0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 3
1	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 4
1	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	

Memory decoder

- Incomplete decoding

A 19	A 18	A 17	A 16	A 15	A 14	A 13	A 12	A 11	A 10	A9	A8	A7	A6	A5	A4	A3	A2	A1	C
0	0	0	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 1
0	0	0	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	0	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 2
0	1	0	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	0	0	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 3
1	0	0	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	1	0	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 4
1	1	0	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	

Memory decoder

- Complete decoding selection functions
 - $\text{/SEL}_{C1} = \text{/A19} * \text{/A18} * \text{/A17} * \text{/A16}$
 - $\text{/SEL}_{C2} = \text{/A19} * \text{A18} * \text{/A17} * \text{/A16}$
 - $\text{/SEL}_{C3} = \text{A19} * \text{/A18} * \text{/A17} * \text{/A16}$
 - $\text{/SEL}_{C4} = \text{A19} * \text{A18} * \text{/A17} * \text{/A16}$
- Incomplete decoding selection functions (removing A16)
 - $\text{/SEL}_{C1} = \text{/A19} * \text{/A18} * \text{/A17}$
 - $\text{/SEL}_{C2} = \text{/A19} * \text{A18} * \text{/A17}$
 - $\text{/SEL}_{C3} = \text{A19} * \text{/A18} * \text{/A17}$
 - $\text{/SEL}_{C4} = \text{A19} * \text{A18} * \text{/A17}$

Memory decoder

- Incomplete decoding
 - Each memory circuit will have 2 address ranges within the processor's address space
 - C1
 - 00000H – 0FFFFH,
 - 10000H – 1FFFFH,
 - Identify the incomplete decoding addresses of C2-4

Memory decoder

- Incomplete decoding

A 19	A 18	A 17	A 16	A 15	A 14	A 13	A 12	A 11	A 10	A9	A8	A7	A6	A5	A4	A3	A2	A1	C
0	0	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 1
0	0	X	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
0	1	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 2
0	1	X	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	0	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 3
1	0	X	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	
1	1	X	X	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	C 4
1	1	X	X	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	

Memory decoder


- Complete decoding selection functions
 - $\text{/SEL}_{C1} = \text{/A19} * \text{/A18} * \text{/A17} * \text{/A16}$
 - $\text{/SEL}_{C2} = \text{/A19} * \text{A18} * \text{/A17} * \text{/A16}$
 - $\text{/SEL}_{C3} = \text{A19} * \text{/A18} * \text{/A17} * \text{/A16}$
 - $\text{/SEL}_{C4} = \text{A19} * \text{A18} * \text{/A17} * \text{/A16}$
- Incomplete decoding selection functions (removing A17 and A16)
 - $\text{/SEL}_{C1} = \text{/A19} * \text{/A18}$
 - $\text{/SEL}_{C2} = \text{/A19} * \text{A18}$
 - $\text{/SEL}_{C3} = \text{A19} * \text{/A18}$
 - $\text{/SEL}_{C4} = \text{A19} * \text{A18}$

Memory decoder

- Incomplete decoding
 - Each memory circuit will have 4 address ranges within the processor's address space
 - C1
 - 00000H – 0FFFFH,
 - 10000H – 1FFFFH,
 - 20000H – 2FFFFH,
 - 30000H – 3FFFFH.
 - Identify the incomplete decoding addresses of C2-4


Memory decoder

- Complete decoder implementation
 - $\overline{\text{SEL}}_{C1} = \overline{A19} * \overline{A18} * \overline{A17} * \overline{A16}$ (0000)
 - $\overline{\text{SEL}}_{C2} = \overline{A19} * A18 * \overline{A17} * \overline{A16}$ (0100)
 - $\overline{\text{SEL}}_{C3} = A19 * \overline{A18} * \overline{A17} * \overline{A16}$ (1000)
 - $\overline{\text{SEL}}_{C4} = A19 * A18 * \overline{A17} * \overline{A16}$ (1100)

 

Memory decoder

 - Incomplete decoder implementation
 - $\overline{\text{SEL}}_{C1} = \overline{A19} * \overline{A18}$ (00)
 - $\overline{\text{SEL}}_{C2} = \overline{A19} * A18$ (01)
 - $\overline{\text{SEL}}_{C3} = A19 * \overline{A18}$ (10)
 - $\overline{\text{SEL}}_{C4} = A19 * A18$ (11)



Memory decoder

- Complete decoding vs. incomplete decoding
 - Complete decoding assumes one and only one address range for a memory block
 - Incomplete decoding allows more than one address range for a memory block
 - Incomplete decoding may simplify the implementation of the decoder
 - Complete decoding allows the efficient usage of the microprocessor address space
 - Incomplete decoding is used for small size memory requirements
 - Incomplete decoding design has low scalability and extensibility

Data transfers

- Memory map - summary
 - Memory circuits parameters
 - Number of circuits
 - Divide the amount of required memory size by the size of the available circuits
 - » $64 \text{ kB} / 16 \text{ kB} = 4 \text{ circuits}$
 - Number of blocks
 - Group circuits together in one block so that the memory will provide the maximum data size required by the processor in one transaction (size of the data bus)
 - Divide processor's data width by memory data lines to calculate the number of the circuits needed in one block
 - » $16 / 8 = 2 \text{ circuits in one block}$
 - » 2 blocks of 2 circuits each
 - » 1 block has 32 kB


Data transfers

- 16 bits processors have to implement both:
 - 16 bits transfers
 - 8 bits transfers
- 8086: /BHE and A₀

$\overline{\text{BHE}}$	A₀	Characteristics
0	0	Whole word
0	1	Upper byte from/to odd address
1	0	Lower byte from/to even address
1	1	None

Data transfers

 - 16 bits transfers – even address ($A0 = 0$, $/BHE = 0$)
- 8 bits transfers
 - Odd address ($A0 = 1$, $/BHE = 0$)
 - Even address ($A0 = 0$, $/BHE = 1$)



Summary

- Bus
 - Amplifying bus lines
 - Demultiplexing bus lines
 - Decoding address lines
 - Data transfers

