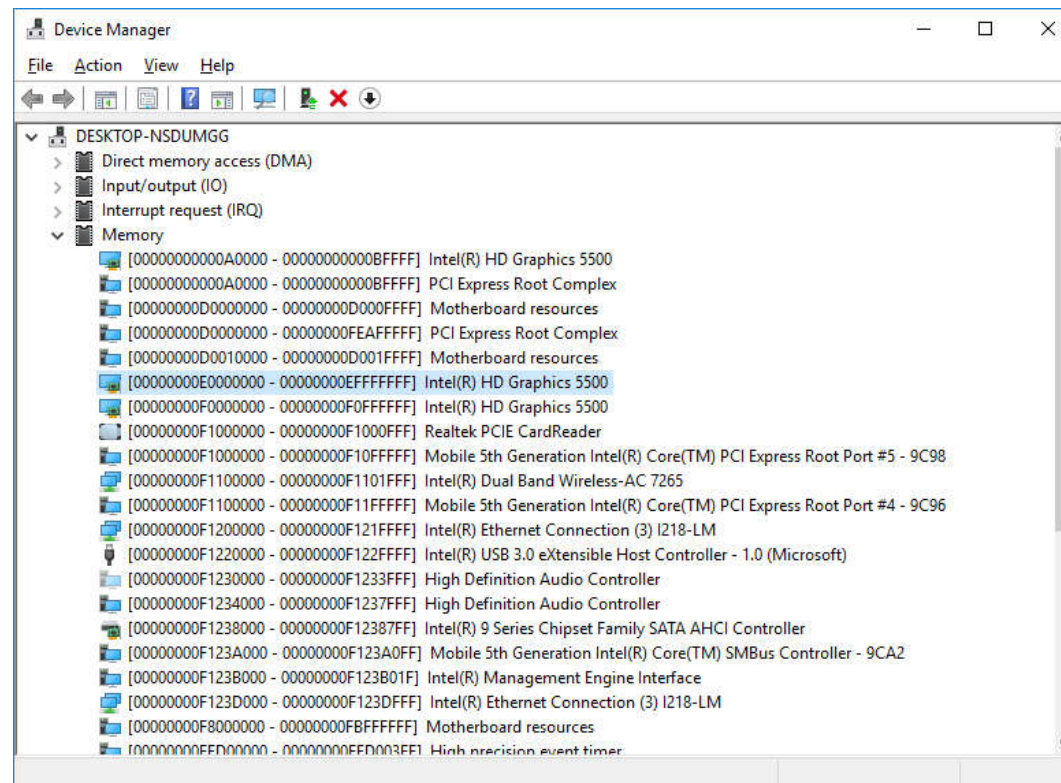


Digital microsystems design

Lab 3

Memory map

- x86/x64




Exercise

- Design the memory map for a 32 bits microprocessor system with 32 address lines using the following memory requirements:
 - 512 MB EEPROM, using 128 M x 16 bits memories
 - 1 GB SRAM, using 64 M x 32 bits memories
 - 2 GB DRAM, using 256 M x 8 bits memories

Overview

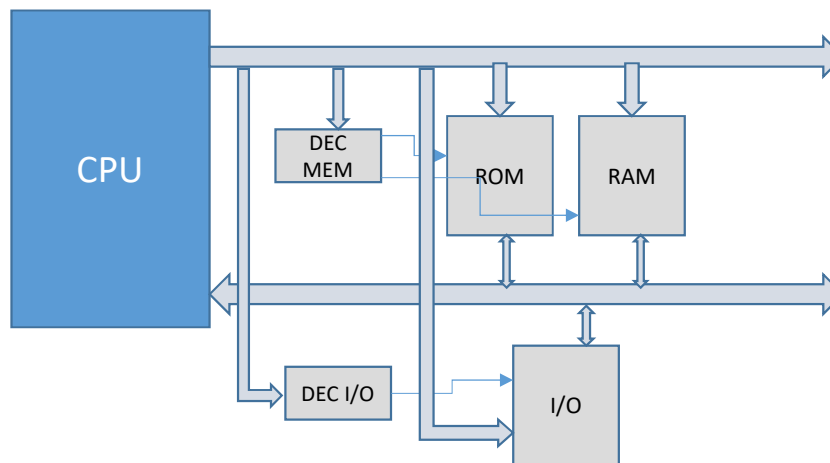- External connectivity of a microprocessor
 - Memory / I/O connectivity



Step 0

- How much memory the processor can access?
 - Max amount of memory = $2^{\text{address bus width of the processor}}$
 - $2^{32} = 2^2 \times 2^{30} = 4 \text{ GB}$
 - Address space of the processor:
 - 0000_0000h – FFFF_FFFFh

Step 1

- How many circuits are needed?
 - No of circuits = size of the required memory / size of the available memory circuits
 - No of EEPROM circuits = $512 \text{ MB} / (128 \text{ M} \times 16 \text{ bits}) =$
 $= 512 \text{ MB} / 256 \text{ MB} = 2$
 - No of SRAM circuits = ...
 - No of DRAM circuits = ...

Step 2

- How many memory blocks are required?
 - Circuits have to be grouped into blocks in order to match the data bus width of the processor
 - No of circuits per bloc = processor data bus width / memory data bus width
 - No of blocks = no of circuits / no of circuits per block
 - No of EEPROM circuits per block = $32 / 16 = 2$
 - No of EEPROM blocks = $2 / 2 = 1$
 - No of SRAM blocks ...
 - No of DRAM blocks ...

Step 3

- Visualize the systems (block diagram)


Data transfers

- 16 bits processors have to implement both:
 - 16 bits transfers
 - 8 bits transfers
- 8086: /BHE and A₀

$\overline{\text{BHE}}$	A₀	Characteristics
0	0	Whole word
0	1	Upper byte from/to odd address
1	0	Lower byte from/to even address
1	1	None


Data transfers

 - 16 bits transfers – even address ($A0 = 0$, $/BHE = 0$)
- 8 bits transfers
 - Odd address ($A0 = 1$, $/BHE = 0$)
 - Even address ($A0 = 0$, $/BHE = 1$)




Data transfer

 - 32 bits data bus
 - 32 bits transfers
 - 16 bits transfers
 - 8 bits transfers




Data transfer

 - Hardware organization of physical address space (32 bits)
 - 32 bits memory block




Data transfer

- 1 byte
 - Address $4xk$

 


- Address $4xk+1$

 


Data transfer

 - 1 word
 - Address $4xk$
- 1 double word
 - Address $4xk$



Data transfer

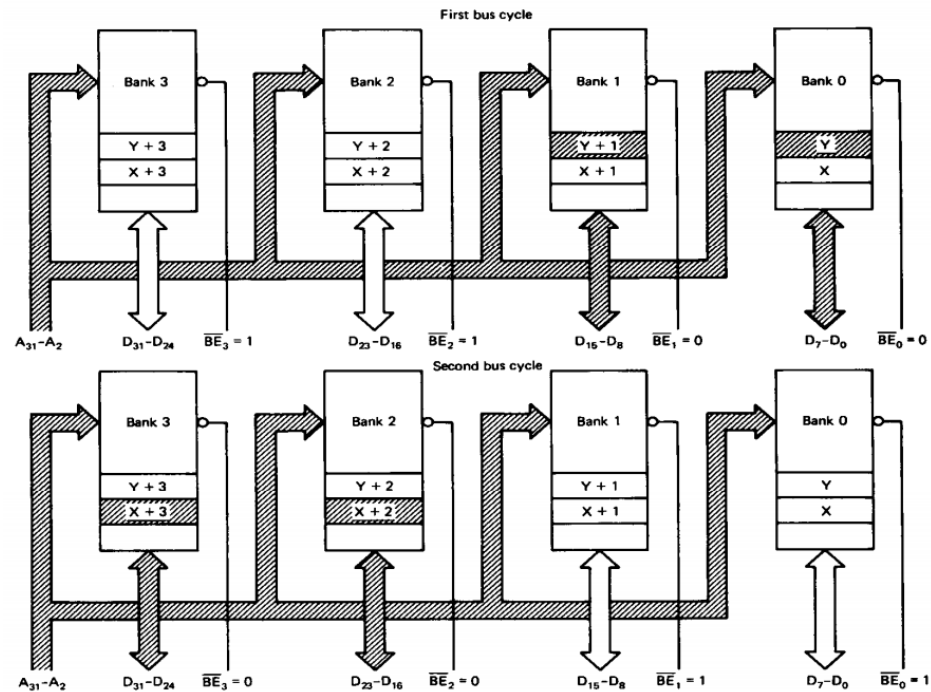- Misaligned double-word data transfer
 - Address $4xk+2$ – the processor will perform 2 bus cycles



Step 4

- Characterize each block
 - Selection is made at block level, not at the circuit level
 - Size, number of address lines, range of addresses
- EEPROM block: $512 \text{ MB} = 2^9 \times 2^{20} = 2^{29}$
 - 29 address lines
 - Size of the block: $2^{29} = 1 \underbrace{000\dots00}_{29 \text{ of } 0} = 200000000 \text{ H}$
- Address range: $0000_0000\text{H} - 1\text{FFF_FFFFH}$

Step 4

- Characterize each block
 - SRAM

Step 4

- Characterize each block
 - DRAM

Step 5

- Memory map

Solution

```
EPROM
no of blocks = 1
B1

512 MB = 2000_0000h

SRAM = 4 circuits
no of circuit per block = 32 / 32 = 1
no of SRAM blocks = 4 / 1 = 4
B2, B3, B4, B5

256 MB = 2^8 * 2^20 = 2^28 = 1000_0000h

DRAM = 8 circuits
no of circuits per block = 32 / 8 = 4
no of DRAM blocks = 8 / 4 = 2
B6, B7

4 * 256 MB = 1 GB = 2^30 = 4000_0000h
```

Memory map

	Start address	-	Ending address
B1	0000_0000h	-	1FFF_FFFFh
B2	2000_0000h	-	2FFF_FFFFh
B3	3000_0000h	-	3FFF_FFFFh
B4	4000_0000h	-	4FFF_FFFFh
B5	5000_0000h	-	5FFF_FFFFh
B6	8000_0000h	-	BFFF_FFFFh
B7	C000_0000h	-	FFFF_FFFFh

Next

- Decoding table
- Memory decoder