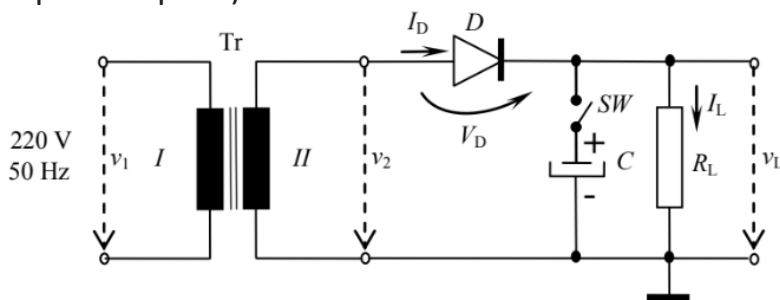


THE HALF WAVE RECTIFIER

❖ Theoretical Summary

A rectifier is a device that converts the sinusoidal alternating current (AC) into somewhat constant direct current (DC). Half wave rectifiers converts only one half-cycle of the AC voltage (positive in our case) and will block the other half.

The half wave rectifier is connected to a sinusoidal AC voltage source of 220V RMS and 50Hz through a step-down transformer, that steps the voltage down to $\approx 13.3\text{V RMS}$ ($\approx 37.8\text{V}$ peak to peak).



• Components

a. *Tr – Step-Down Transformer*

- used to lower the voltage between the 2 circuits, while also increasing the current by the same factor
- N_1 – nr. of coil turns from I
- N_2 – nr. of coil turns from II ($< N_1$)
- V_{1m} – voltage amplitude of I
- V_{2m} – voltage amplitude of II
- $n = \frac{N_1}{N_2} = \frac{V_{1m}}{V_{2m}}$ – transformation ratio

b. *D – Diode*

- constitutes the rectifier of the circuit
- allows current to pass only in one direction, the positive half of the input sinusoidal wave

c. *C – Capacitor*

- makes up the low-pass filter
- used to smoothen the pulsating DC waveform

d. *RL – Load Resistor*

• Values

- $R_L = 5\text{k}\Omega$
- C – cases:
 - i. No capacitor
 - ii. 1 capacitor – $C = 22\mu\text{F}$
 - iii. 2 capacitors in parallel – $C = 44\mu\text{F}$
 - iv. 3 capacitors in parallel – $C = 66\mu\text{F}$
 - v.

• Formulas

- $V_m = \frac{V_{pp}}{2}$

- $T = \frac{1}{f}$
- $V_{LDC} = \frac{V_{2m}}{\pi}$ (no capacitor)
- $\Delta v_L = \frac{V_{2m}}{C \cdot R \cdot f}$, $V_{LDC} = V_{2m} - \frac{\Delta v_L}{2}$ (with capacitor)

❖ **Experimental Procedure**

- make the circuit above
- using a multimeter (VAC domain), it is measured the voltage given by the transformer secondary -> amplitude ($A = V_{2m}$) & time period (T)
- For the 4 cases: SW open, SW closed(1C, 2C & 3C):
 - output waveform $v_L(t)$ is observed
 - measurements are took for the DC component of the output voltage V_{LDC} and the ripple Δv_L

❖ **Measurements – taken from screenshots of oscilloscope(lab 3)**

- $f = 50Hz \Rightarrow T = 20 ms = 0.02s$

▪ **Case I – No C**

$$V_{2pp} = 37.8V \Rightarrow V_{2m} = \frac{37.8}{2} = 18.9V$$

$$V_{LDC} = 5.80V$$

▪ **Case II – 1 C**

$$V_{2pp} = 37.4V \Rightarrow V_{2m} = \frac{37.4}{2} = 18.7V$$

$$\Delta v_L = 1.88V$$

$$V_{LDC} = 17.76V$$

▪ **Case III – 2 C**

$$V_{2pp} = 37.4V \Rightarrow V_{2m} = \frac{37.4}{2} = 18.7V$$

$$\Delta v_L = 1.1V$$

$$V_{LDC} = 18.15V$$


▪ **Case IV – 3 C**

$$V_{2pp} = 37.4V \Rightarrow V_{2m} = \frac{37.4}{2} = 18.7V$$


$$\Delta v_L = 0.74V$$

$$V_{LDC} = 18.33V$$


CASE I

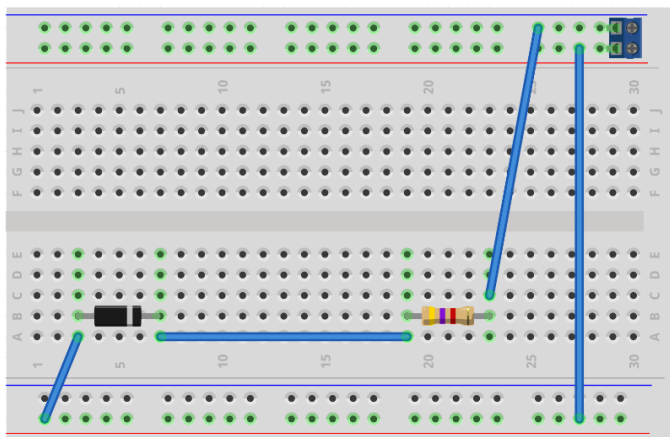


Redresor monoalternanță
Fără filtru capacitiv

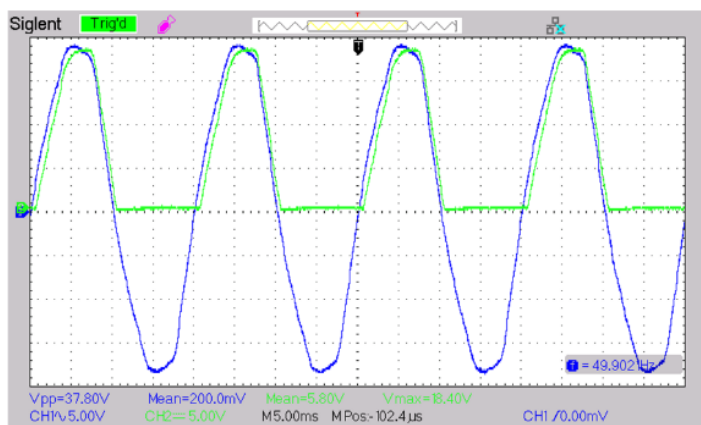


CASE II

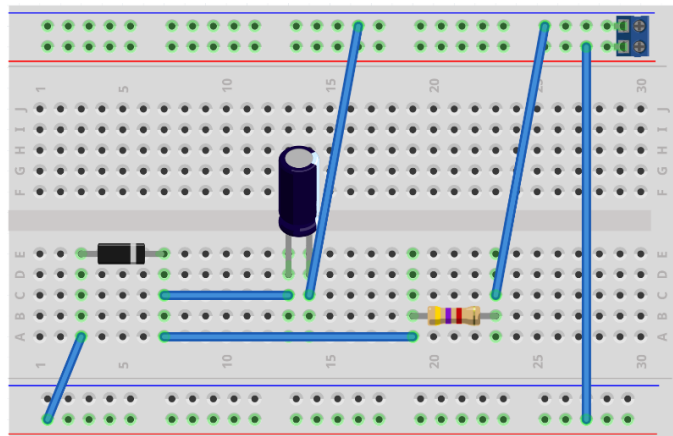


Redresor monoalternanță
Cu filtru capacitiv - doar ondulația C=22 μF

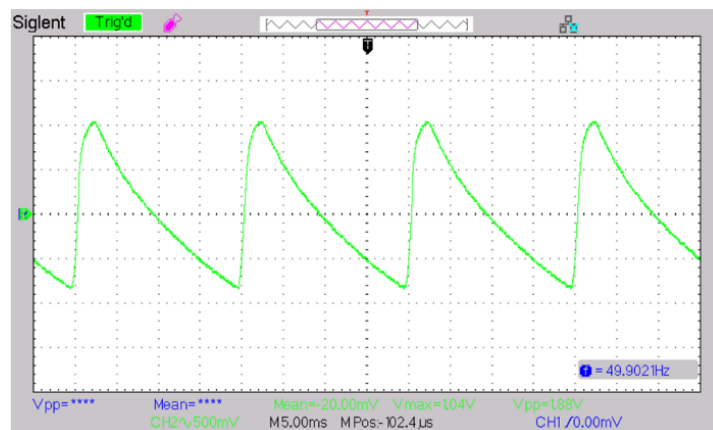


CASE III

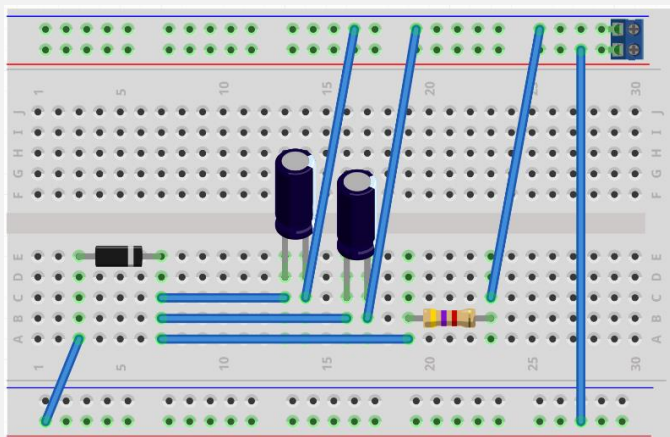

Redresor monoalternanță
Cu filtru capacitiv - doar ondulația C=44 μF

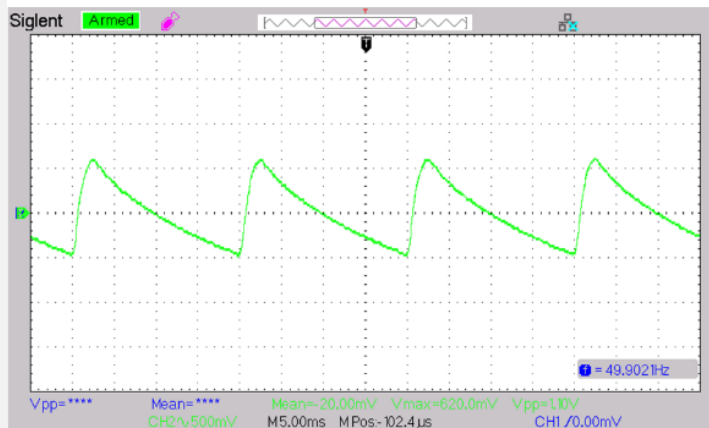

CASE IV

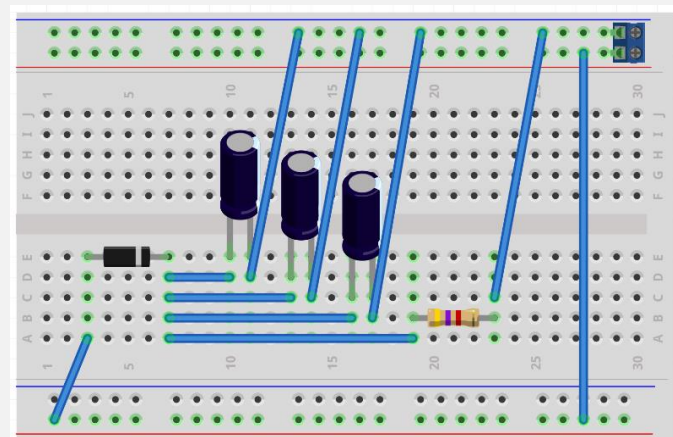

Redresor monoalternanță
Cu filtru capacitiv - doar ondulația C= 66 μF



❖ Calculations

- $V_{2pp} = 37.8V \Rightarrow V_{2m} = \frac{37.8}{2} = 18.9V$
- $f = 50Hz \Rightarrow T = 20ms = 0.02s$

▪ Case I – No C

$$V_{LDC} = \frac{18.9}{\pi} = 6.02V$$

▪ Case II – 1 C

$$\Delta v_L = \frac{18.9}{22 \cdot 5 \cdot 50 \cdot 10^{-3}} = 3.44V$$

$$V_{LDC} = 18.9 - \frac{3.44}{2} = 17.18V$$

▪ Case III – 2 C

$$\Delta v_L = \frac{18.9}{44 \cdot 5 \cdot 50 \cdot 10^{-3}} = 1.72V$$

$$V_{LDC} = 18.9 - \frac{1.72}{2} = 18.04V$$



▪ Case IV – 3 C

$$\Delta v_L = \frac{18.9}{66 \cdot 5 \cdot 50 \cdot 10^{-3}} = 1.15V$$



$$V_{LDC} = 18.9 - \frac{1.15}{2} = 18.33V$$

❖ Simulations



CASE I

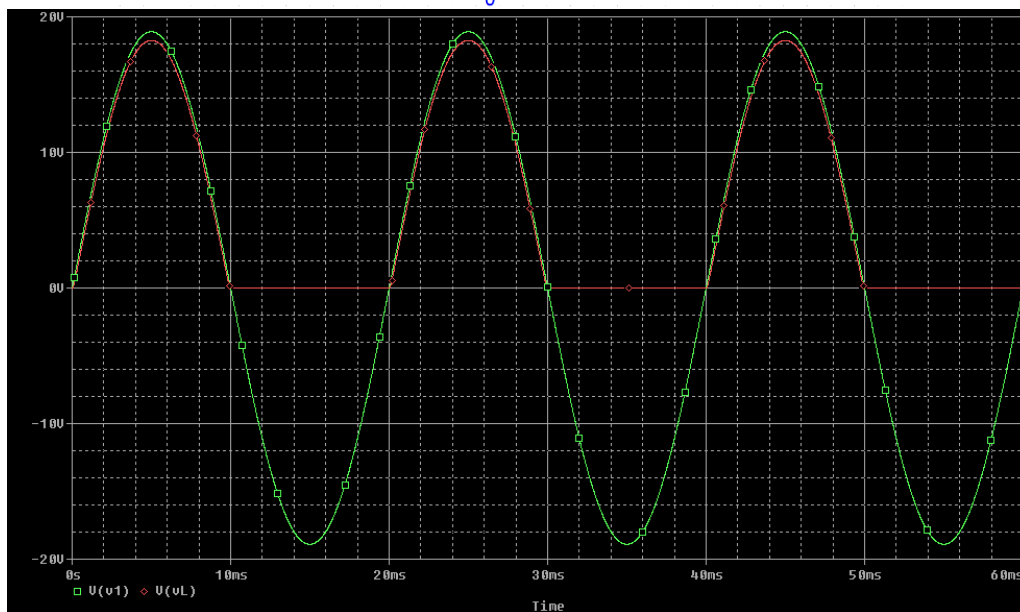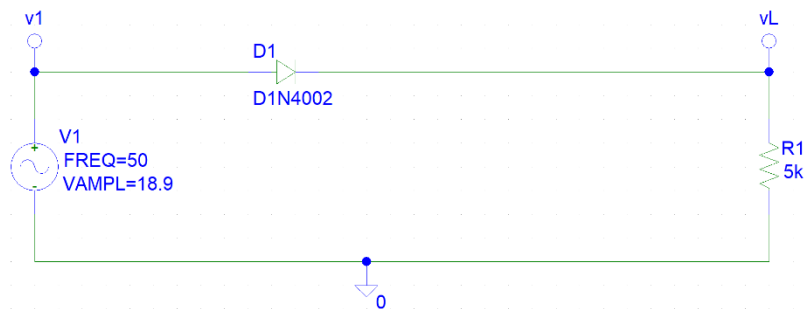



CASE II

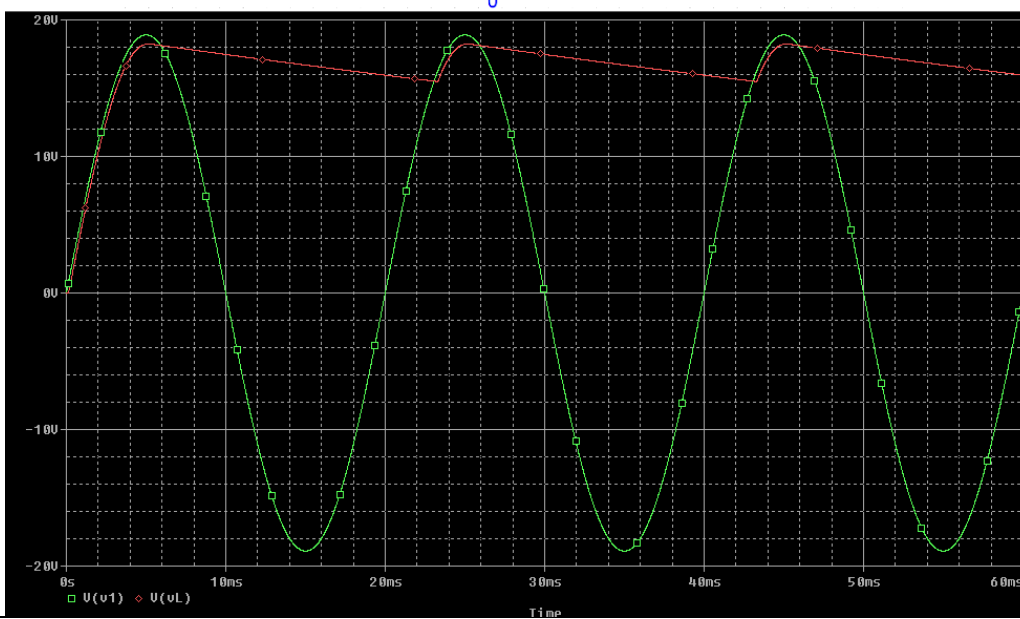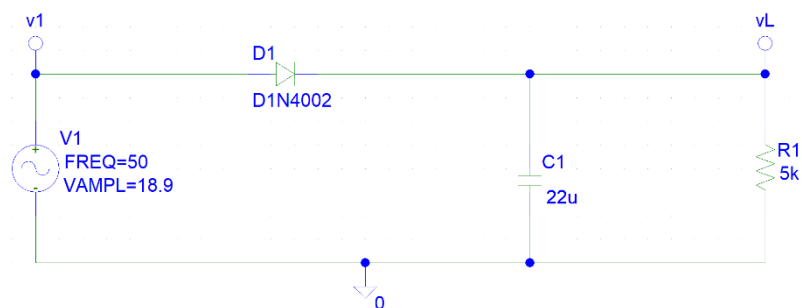

CASE III

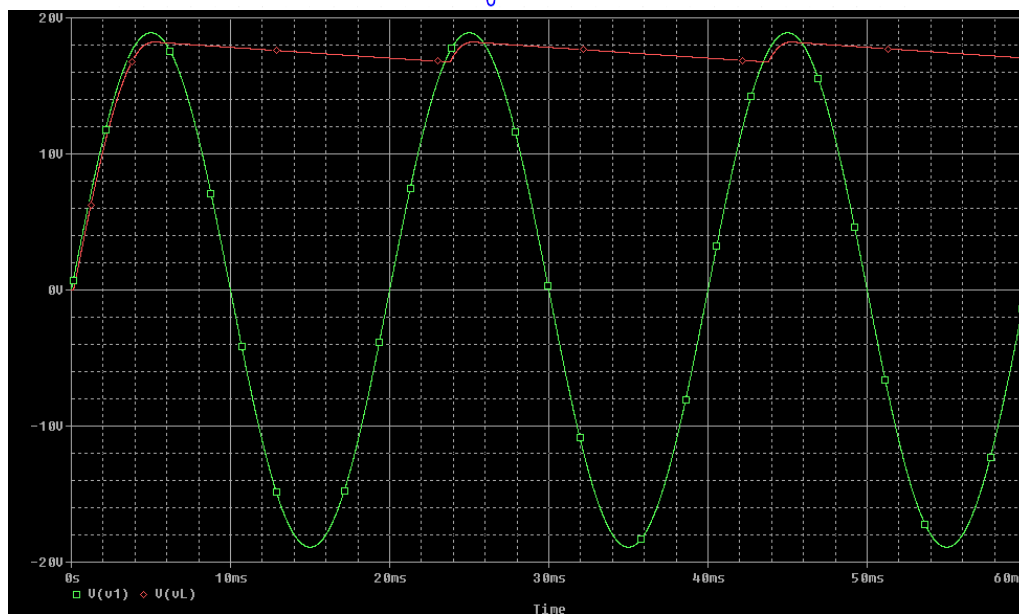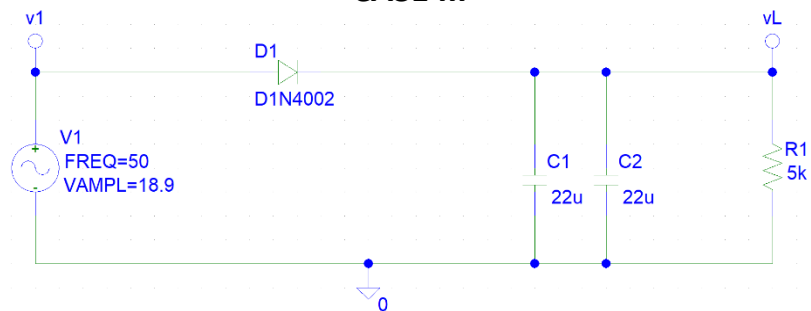

CASE IV

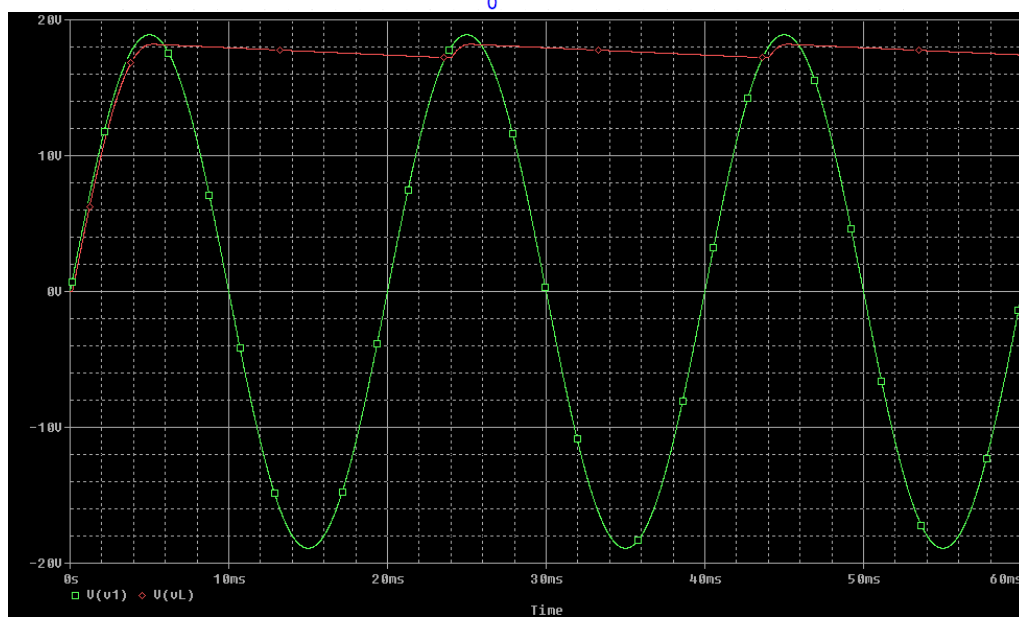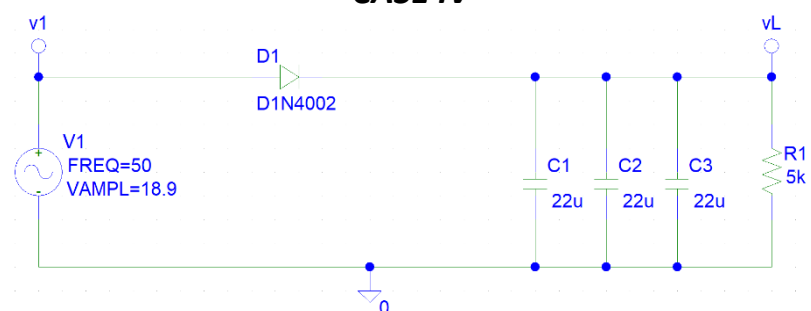

❖ **Tables**

▪ **Experimental**

CAPACITORS	V_{2m}	Δv_L	V_{LDC}
0	18.9	-	5.80
1	18.7	1.88	17.76
2	18.7	1.11	18.15
3	18.7	0.74	18.33

▪ **Calculation**

CAPACITORS	Δv_L	V_{LDC}
0	-	6.02
1	3.44	17.18
2	1.72	18.04
3	1.15	18.33

❖ **Conclusion**

Following the experiments & calculations, we can conclude that with the increase in capacitors, the output DC voltage also increases and the ripple decreases, smoothing the DC waveform.