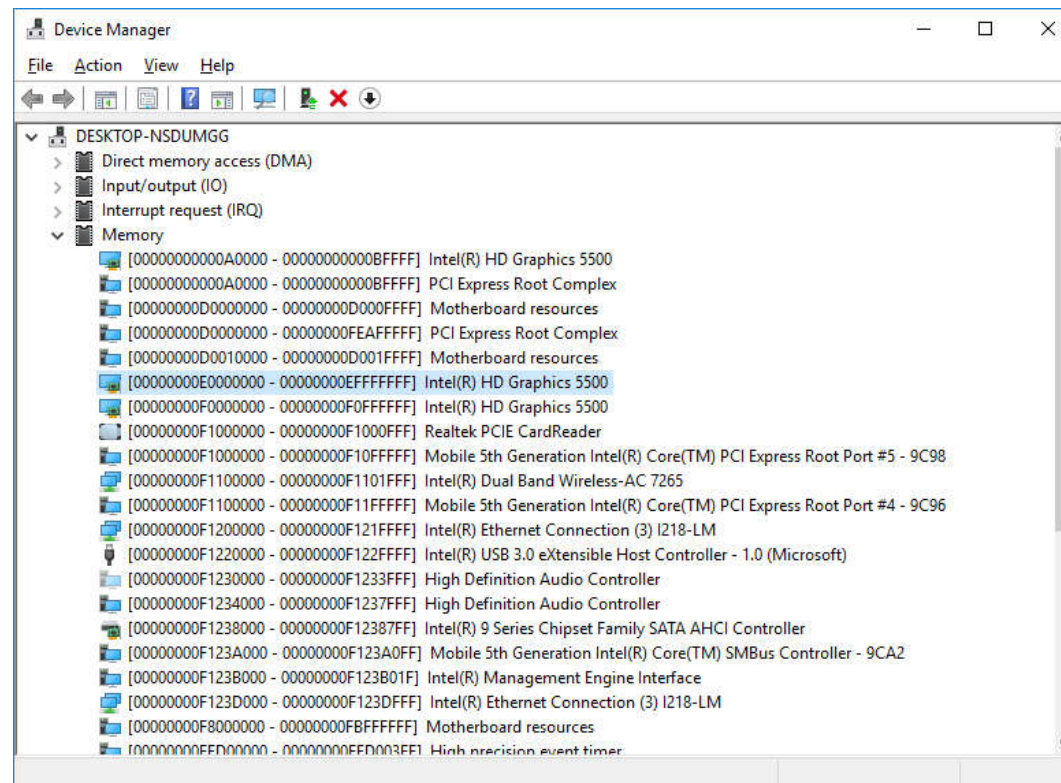


Digital microsystems design

Lab 2

Memory map

- x86/x64




Exercise

- Design the memory map and memory decoder for a 16 bits microprocessor system with 20 address lines using the following memory requirements:
 - 128KB EEPROM ending at FFFFFH, using 64K x 16 bits memories
 - 128KB SRAM starting at 00000, using 64K x 16 bits memories
 - 128KB DRAM, using 32K x 16 bits memories

Overview

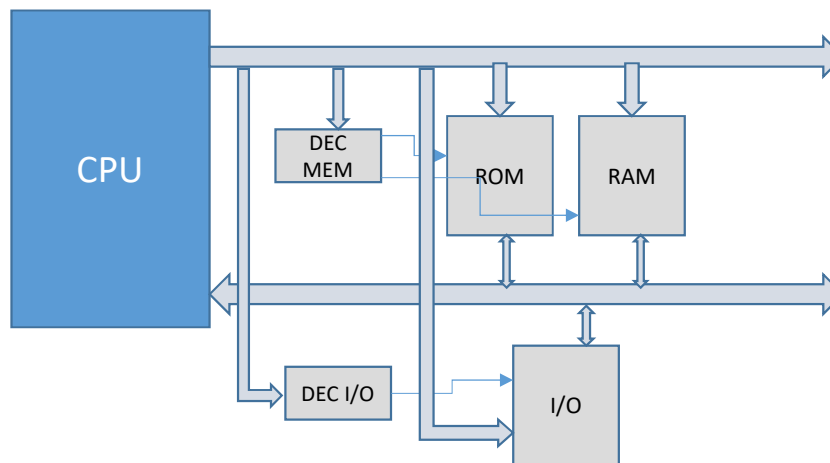- External connectivity of a microprocessor
 - Memory / I/O connectivity



Step 1

- How many circuits are needed?
 - No of circuits = size of the required memory / size of the available memory circuits
 - No of EPROM circuits = $128 \text{ KB} / (64 \text{ K} \times 16 \text{ bits}) =$
 $= 128 \text{ KB} / 128 \text{ KB} = 1$
 - No of SRAM circuits = ...
 - No of DRAM circuits = ...

Step 2

- Visualize the systems (block diagram)

Step 3

- Characterize each circuit
 - Size, number of address lines, range of addresses

- EPROM circuit: $128 \text{ KB} = 2^7 \times 2^{10} = 2^{17}$

- 17 address lines

$$2^{17} = 1 \underbrace{000 \dots 00}_{17 \text{ of } 0} = 20000 \text{ H}$$

17 of 0

- Address range: 00000H – 1FFFFH

Step 4

- Memory map