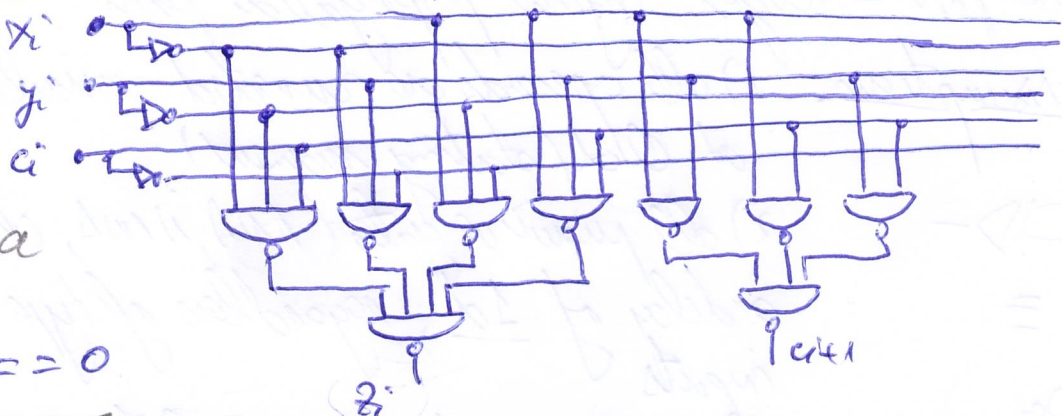


CH 5 ① NAND gates

$a \oplus 0 = a$




C_0 can be 0: $C_0 = 0$

$z_0 = x_0 \oplus y_0 \oplus c_0 = x_0 \oplus y_0$

$c_1 = x_0 y_0 + x_0 \cdot 0 + y_0 \cdot 0 = x_0 \cdot y_0$

HAC's synthesis

① EXOR - AND

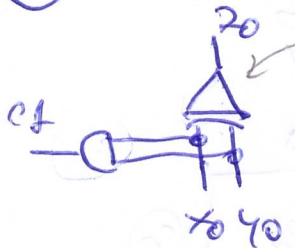


③ NOR gates

$a \oplus b = \overline{a}b + a\overline{b}$
 $a \cdot \overline{a} = 0$

$z_0 = x_0 \oplus y_0 = x_0 \overline{y_0} + \overline{x_0} y_0 =$
 $= x_0(\overline{x_0} + \overline{y_0}) + y_0(\overline{x_0} + \overline{y_0}) =$

$= \overline{(x_0 + y_0)(\overline{x_0} + \overline{y_0})} = \overline{x_0 + y_0} + \overline{\overline{x_0} + \overline{y_0}}$

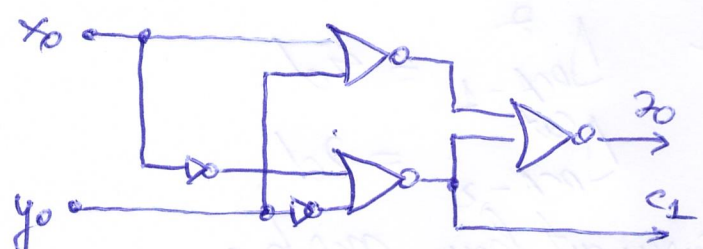$z_1 = \overline{x_0 \cdot y_0} = \overline{x_0 + y_0}$




$\overline{x_0 + y_0} = \overline{x_0 \cdot y_0}$

② NAND gates

$z_0 = x_0(\overline{x_0} + \overline{y_0}) + y_0(\overline{x_0} + \overline{y_0}) =$


$c_1 = \overline{x_0 \cdot y_0}$

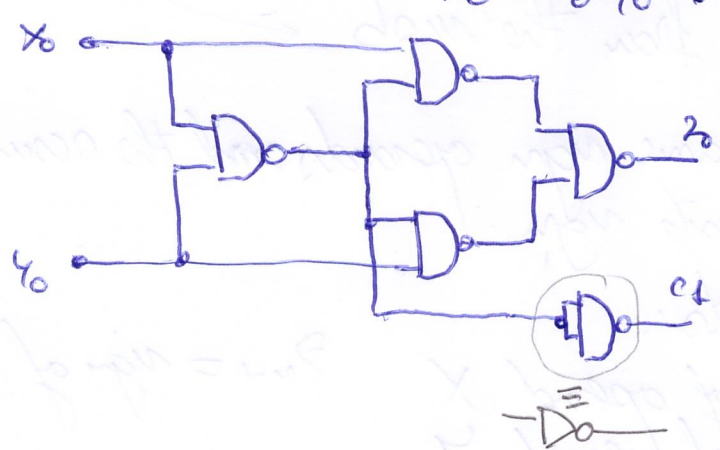$= \overline{x_0 \cdot \overline{x_0 \cdot y_0} \cdot y_0 \cdot \overline{x_0 \cdot y_0}}$



Critical path = longest signal propagation path

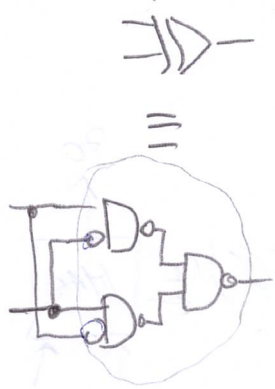Assumptions: 1) all operands are connected simultaneously at 0d (starting moment)




2) all primitive gates (AND, OR, NOR, XOR) have a delay of 1d, regardless of type and number of inputs

3) EXOR gates have a latency of 2d

4) inverters are delay-free

RCA on n bits

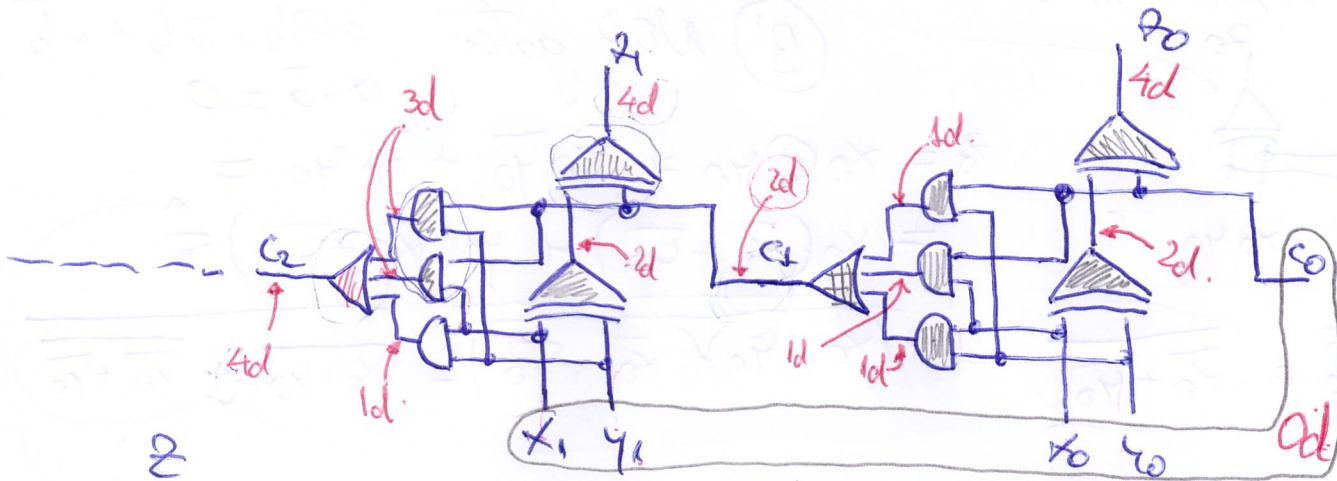

$$\Delta_{RCA-n} = 2nd$$

$$\Delta_{RCA-n}^{Car} = 2nd$$

Exception

$$\Delta_{RCA-1} = 4d$$

$$\Delta_{RCA-2}^{Car} = 2d$$

Addition's special conditions:

- Carry out from msb
- Zero result
- Negative result
- Overflow

notation
V = overflow

- V → unsigned numbers: carry out from the msb
- V → signed numbers: adding same sign operands and the result has opposite sign

Consider the sign bits:

- X_{n-1} — sign of operand X
- Y_{n-1} — sign of operand Y

Z_{n-1} = sign of result

Boolean identities

(2)

Input			Output	
X_{n-1}	Y_{n-1}	C_{n-1}	Z_{n-1}	V
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0

$$I_1: (A \oplus B) \cdot C = A \oplus B \cdot C$$

$$I_2: A + B = A \oplus B \oplus AB$$

$$I_2': A \oplus B = (A + B) \oplus AB$$

$$\overline{C_{n-1}} = C_{n-1} \oplus 1$$

$$0 \oplus 0 = 0$$

$$V = \overline{X_{n-1}} \overline{Y_{n-1}} C_{n-1} + X_{n-1} Y_{n-1} \overline{C_{n-1}} =$$

$$\overline{X_{n-1}} \overline{Y_{n-1}} C_{n-1} \oplus X_{n-1} Y_{n-1} \overline{C_{n-1}} \oplus \overline{X_{n-1}} \overline{Y_{n-1}} C_{n-1} X_{n-1} Y_{n-1} \overline{C_{n-1}} =$$

$$\overline{X_{n-1}} \overline{Y_{n-1}} C_{n-1} \oplus X_{n-1} Y_{n-1} \overline{C_{n-1}} \stackrel{I_1}{=} \overline{X_{n-1}} \overline{Y_{n-1}} C_{n-1} \oplus X_{n-1} Y_{n-1} C_{n-1} \oplus I_2'$$

$$(\overline{X_{n-1}} \overline{Y_{n-1}} \oplus X_{n-1} Y_{n-1}) C_{n-1} \oplus X_{n-1} Y_{n-1} \stackrel{I_2'}{=}$$

$$(\overline{X_{n-1}} \overline{Y_{n-1}} + X_{n-1} Y_{n-1}) C_{n-1} \oplus X_{n-1} Y_{n-1} \stackrel{I}{=}$$

$$X_{n-1} \oplus Y_{n-1} = X_{n-1} \oplus Y_{n-1} \oplus 1$$


$$(X_{n-1} \oplus Y_{n-1} \oplus 1) \cdot C_{n-1} \oplus X_{n-1} Y_{n-1} \stackrel{I_1}{=}$$

$$X_{n-1} C_{n-1} \oplus Y_{n-1} C_{n-1} \oplus X_{n-1} Y_{n-1} \oplus C_{n-1} \stackrel{I_2'}{=}$$

$$(\underbrace{X_{n-1} C_{n-1} + Y_{n-1} C_{n-1} + X_{n-1} Y_{n-1}}_{C_n}) \oplus C_{n-1} \Rightarrow$$

$$V = C_n \oplus C_{n-1}$$

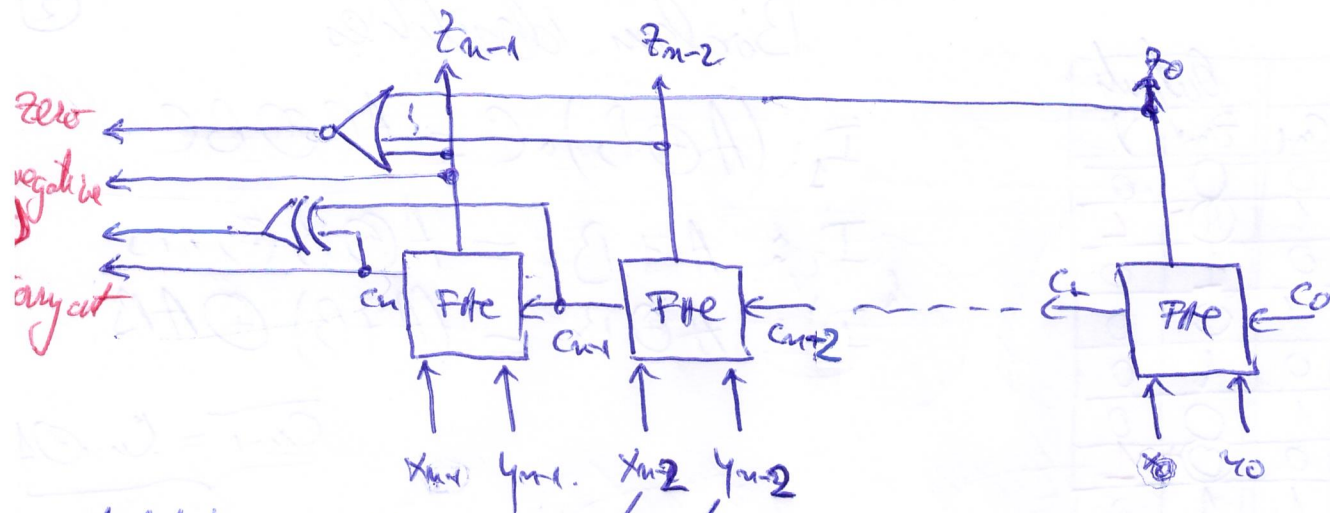Adder with special evolution generator.
- operands are n bits.



Addition with a constant.

- odd constants

- Y operand is the constant

Let X, Y - an n bits.

$Y = y_{n-1} y_{n-2} \dots y_1 y_0$ - constant.


$$X = x_3 x_2 x_1 x_0$$

$$Y = \begin{matrix} 1 & 1 & 0 & 0 \end{matrix}$$


(const)

$$Z = z_3 z_2 z_1 z_0$$

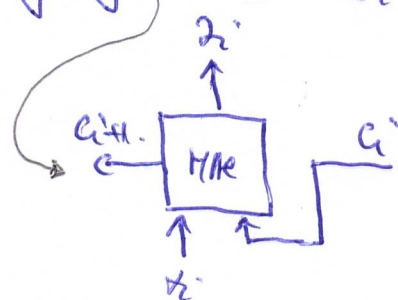if $y_i = 0$: $x_i + y_i + c_i \rightarrow z_i = x_i \oplus 0 \oplus c_i = x_i \oplus c_i$
 $c_{i+1} = x_i \cdot 0 + 0 \cdot c_i + x_i \cdot c_i = x_i \cdot c_i$ } HAE



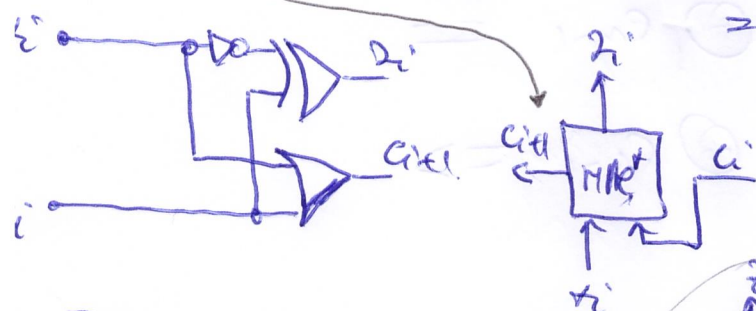if $y_i = 1$: $x_i + y_i + c_i \rightarrow z_i = \overline{x_i} \oplus 1 \oplus c_i = \overline{x_i} \oplus c_i$
 $c_{i+1} = \overline{x_i} \cdot 1 + 1 \cdot c_i + \overline{x_i} \cdot c_i = \overline{x_i} + c_i + \overline{x_i} \cdot c_i = \overline{x_i} + c_i$ (absorbed) } HAE*



Ex: X, Y - an 5 bits.

$$X = x_4 x_3 x_2 x_1 x_0$$


$$Y = \begin{matrix} 1 & 1 & 0 & 1 & 0 \end{matrix}$$

odd const.

$$Z = z_4 z_3 z_2 z_1 z_0$$

$$z_1 = x_1 \oplus 1 \oplus 0 \rightarrow z_1 = x_1 \oplus 1$$
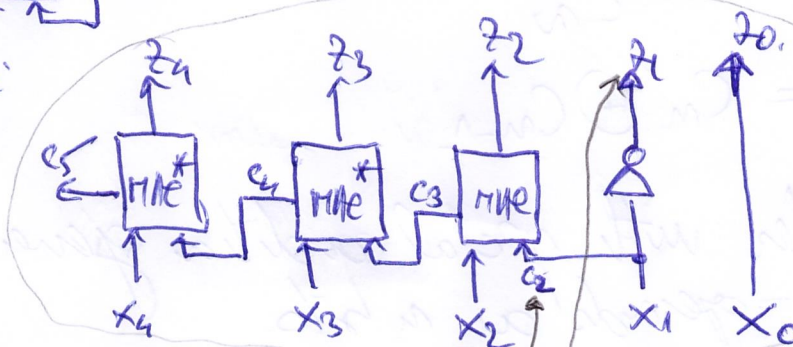
$$c_1 = x_1 \cdot 1 + x_1 \cdot 0 + 1 \cdot 0 = x_1$$



2.2.2. Decimal Adders based on serial carry propagation (3)

- use binary adders for performing BCD addition

④ BCD8421 (BCD) addition.

- on tetrads (= sequence of 4 bits)

$X_i + Y_i \rightarrow Z_i$ X_i, Y_i, Z_i - BCD digits.
 $X_i + Y_i \rightarrow C_{i+1}$ C_{i+1} = carry for digit $i+1$.
 Z_i = sum digit.

$$X_i = x_3 x_2 x_1 x_0$$

$$Z_i = z_3 z_2 z_1 z_0$$

$$Y_i = y_3 y_2 y_1 y_0$$

if $X_i + Y_i < 10 \rightarrow Z_i = X_i + Y_i$
 $C_{i+1} = 0$

if $X_i + Y_i \geq 10 \rightarrow Z_i = X_i + Y_i - 10$
 $C_{i+1} = 1$
 * Z_i needs some correction

carry to next digit

$$\begin{array}{r} 7 \\ + 8 \\ \hline \end{array}$$

$$\begin{array}{r} 15 \\ \hline 10 \end{array}$$

unit's figure

⑤ - sum digit

$X_i + Y_i$ = add 2 ^{binary} 4-bit numbers
 \Rightarrow 5-bit result

$$X_i + Y_i = C^* (z_3^* z_2^* z_1^* z_0^*)$$

$$X_i + Y_i \geq 10 \begin{cases} 10 \leq C^* z_3^* z_2^* z_1^* z_0^* < 16 \quad (C_1) \\ C^* z_3^* z_2^* z_1^* z_0^* \geq 16 \quad (C_2) \end{cases} \rightarrow \text{logic on}$$

$\therefore 10 \leq C^* z_3^* z_2^* z_1^* z_0^* < 16 \rightarrow C^* = 0$
 $\rightarrow z_3^* z_2^* z_1^* z_0^* \in [10; 15] \rightarrow \text{AND}$

$z_3^* z_2^*$	00	01	11	10
00				
01				
11	1	1	1	1
10			1	1

$$10 \leq z_3^* z_2^* z_1^* z_0^* \leq 15$$

$$\equiv z_3^* \cdot z_2^* + z_3^* \cdot z_1^*$$

$$(C_1): \overline{C^*} (z_3^* \cdot z_2^* + z_3^* \cdot z_1^*)$$

$$C_2: (C^* \oplus_3 Z_1^* \oplus_3 Z_2^*) \geq 16 \Rightarrow C^* = 1 \quad \text{absorbed.}$$

$$X_i + Y_i \geq 10 \equiv (C_1) + (C_2) = \overline{C^*} (Z_3^* Z_2^* + Z_2^* Z_1^*) + C^*$$

or

$$X_i + Y_i \geq 10 \equiv [C^* + Z_3^* Z_2^* + Z_2^* Z_1^*]$$

Subtracting 10 from $X_i + Y_i$

if $X_i + Y_i \geq 10$ $Z_i = X_i + Y_i - 10$
 $Z_i =$ on 4 bits.

$$a \bmod b = (a+b) \bmod b.$$

$$\Rightarrow Z_i = (X_i + Y_i - 10) \bmod 2^4$$

$$= (X_i + Y_i - 10 + 16) \bmod 2^4.$$

$$= (X_i + Y_i + 6) \bmod 2^4.$$

$$\begin{array}{r} 15 - \\ 10 \\ \hline 0101 \\ \hline \end{array}$$

$$\begin{array}{r} 1111 + \\ 0110 \\ \hline 0101 \\ \hline \end{array}$$

$$\begin{array}{r} 15 + \\ 6 \\ \hline \end{array}$$

Subtract 10 on 4 bits \equiv Add 6 on 4 bits
 $Z_i = Z_3 Z_2 Z_1 Z_0 +$
 0110 *const*

Z_i 's calculation

depends on: $C^* + Z_3^* Z_2^* + Z_2^* Z_1^*$

1

$(X_i + Y_i \geq 10)$

$C_{i+1} = 1$