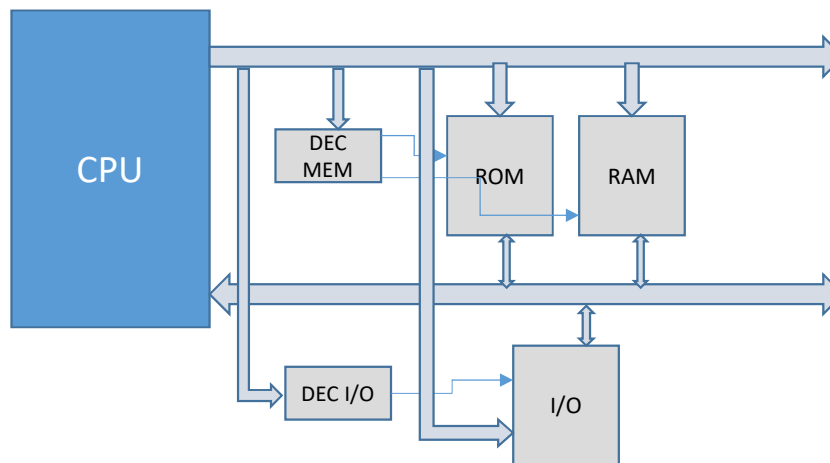


Digital microsystems design

Lab 3

Overview

- External connectivity of a microprocessor
 - Memory / I/O connectivity



Exercise

- Design the memory map and the memory decoder for a 32bits uP system using the following memory requirements:
 - 256MB EPROM ending at FFFFFFFFH, using 64M x 16bits memories
 - 512MB SRAM, using 64M x 8 bits memories
 - 1GB DRAM, using 128M x 4 bits memories, placed as a contiguous memory address space

Solution

- Determine the size of the whole address space of the processor
- Determine the number of memory circuits required by the design
- Determine the number of 32bits blocks and their sizes (in MB and hexa)
- Determine the number of selection lines
- Design the memory map
- Design the memory decoder using a 3-to-8 decoder

Solution

- Determine the size of the whole address space of the processor
 - Max amount of memory = $2^{\text{address bus width of the processor}}$
 - $2^{32} = 2^2 \times 2^{30} = 4 \text{ GB}$
 - Address space of the processor:
 - 0000_0000h – FFFF_FFFFh

Solution

- Determine the number of memory circuits required by the design
 - No of circuits = size of the required memory / size of the available memory circuits
 - No of EEPROM circuits = $256\text{MB} / (64\text{M} \times 16 \text{ bits})$
 $= 256\text{MB} / 128\text{MB} = 2$
 - No of SRAM circuits = $512\text{MB} / 64\text{MB} = 8$
 - No of DRAM circuits = $1\text{GB} / (128\text{M} \times 4)$
 $= 1\text{GB} / (128\text{M} \times 1/2\text{B}) = 1024\text{MB} / 64\text{MB} = 16$

Solution

- Determine the number of 32bits blocks
 - Circuits have to be grouped into blocks in order to match the data bus width of the processor
 - No of circuits per block = processor data bus width / memory data bus width
 - No of blocks = no of circuits / no of circuits per block
 - EEPROM
 - No of EEPROM circuits per block = $32 / 16 = 2$
 - No of EEPROM blocks = $2 / 2 = 1$
 - SRAM
 - No of SRAM circuits per block = $32 / 8 = 4$
 - No of SRAM blocks = $8 / 4 = 2$
 - DRAM
 - No of SRAM circuits per block = $32 / 4 = 8$
 - No of DRAM blocks = $16 / 8 = 2$

Solution

- Determine the size of each block (in MB and hexa)
 - EEPROM
 - Block B1: $2 * 128 \text{ MB} = 256 \text{ MB} = 2^8 * 2^{20} = 2^{28} = 1000_0000\text{h}$
 - SRAM
 - B2: $4 * 64 \text{ MB} = 256 \text{ MB} = 2^{28} = 1000_0000\text{h}$
 - B3: $4 * 64 \text{ MB} = 256 \text{ MB} = 2^{28} = 1000_0000\text{h}$
 - DRAM
 - B4: $8 * 128 \text{ M} \times 4\text{bits} = 512 \text{ MB} = 2^{29} = 2000_0000\text{h}$
 - B5: $8 * 128 \text{ M} \times 4\text{bits} = 512 \text{ MB} = 2^{29} = 2000_0000\text{h}$

Solution

- Visualize the system (block diagram)

Solution


- Memory map
 - B1
 - B2
 - B3
 - B4
 - B5

Solution

- Decoding
 - Decoding circuits
 - 74x138: decoder $3 \rightarrow 8$,
 - 74x139: decoder $2 \times 2 \rightarrow 4$,
 - 74x42: decoder $4 \rightarrow 10$,
 - 74x154: decoder $4 \rightarrow 16$.

Solution

- 74x138 decoder

 

E3	/E2	/E1	A2	A1	A0	/Y7	/Y6	/Y5	/Y4	/Y3	/Y2	/Y1	/Y0
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1
0	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	1	X	X	X	1	1	1	1	1	1	1	1

Solution

- Memory decoder
 - Component of a digital system that generates selection signal for the slave module addressed by in the current bus transaction
 - Inputs: most significant bits of the address bus
 - Outputs: selection signals for each memory module
 - Design steps
 - Memory requirements and constraints
 - Memory setup
 - Memory map
 - Logic design
 - Optimization (speed, space, complexity)

Solution

- Decoding table

A 31	A 30	A 29	A 28	A 27	A 26	A 25	A 24							A4	A3	A2	A1	A0	
																			B1
																			B2
																			B3
																			B4
																			B5

Solution

- Selection functions

Solution

- Memory decoder

