

CS 7.5

2.3.4 Conditional Sum Adder (CSAA)

- principle of *non conditioned by carry*
- generalization of CSA on *multiple levels*
- on multiple levels:
 - first: generate g_i, c_{i+1}
 - subsequent stages: select the correct variant

$c_0 = 0!!!$

$$\begin{aligned}
 c_{i+1} &= x_i \cdot y_i + x_i \cdot a_i + y_i \cdot a_i \\
 &= x_i \cdot y_i (a_i + \bar{a}_i) + x_i \cdot a_i + y_i \cdot a_i = x_i \cdot y_i \cdot \underbrace{a_i + \bar{a}_i}_1 + x_i \cdot a_i + y_i \cdot a_i \\
 &= x_i \cdot y_i \cdot \bar{a}_i + x_i \cdot a_i (\underbrace{y_i + 1}_1) + y_i \cdot a_i \Rightarrow \\
 &= x_i \cdot y_i \cdot \bar{a}_i + x_i \cdot \bar{a}_i + y_i \cdot a_i = \\
 &= x_i \cdot y_i \cdot \bar{a}_i + (x_i + y_i) \cdot a_i
 \end{aligned}$$

$a = a(b + \bar{b})$

$g_i = x_i \cdot y_i$
 $p_i = x_i + y_i$

$c_{i+1} = g_i \cdot \bar{a}_i + p_i \cdot a_i$

$$\begin{aligned}
 \bar{a}_{i+1} &= \overline{g_i \cdot \bar{a}_i + p_i \cdot a_i} = \overline{g_i \cdot \bar{a}_i} \cdot \overline{p_i \cdot a_i} = \\
 &= (\bar{g}_i + a_i)(\bar{p}_i + \bar{a}_i) = \underbrace{\bar{g}_i \bar{p}_i}_{\text{absorbed}} + \bar{g}_i \bar{a}_i + \bar{p}_i \bar{a}_i + \underbrace{a_i \bar{a}_i}_0
 \end{aligned}$$

$\bar{c}_{i+1} = \bar{g}_i \cdot \bar{a}_i + \bar{p}_i \cdot \bar{a}_i$

$a \oplus b = \bar{a} \cdot b + a \cdot \bar{b}$

Let X, Y - 4-bit operands

Sum bits

Carry bits


$$\begin{aligned}
 z_0 &= x_0 \oplus y_0 \oplus c_0 = x_0 \oplus y_0 \\
 z_1 &= x_1 \oplus y_1 \oplus c_1 = \overline{x_1 \oplus y_1} \cdot c_1 + (x_1 \oplus y_1) \cdot \bar{c}_1 \\
 z_2 &= x_2 \oplus y_2 \oplus c_2 = \overline{x_2 \oplus y_2} \cdot c_2 + (x_2 \oplus y_2) \cdot \bar{c}_2
 \end{aligned}$$

$$\begin{aligned}
 c_1 &= g_0 \cdot \bar{c}_0 + p_0 \cdot c_0 = g_0 \\
 c_2 &= g_1 \cdot \bar{c}_1 + p_1 \cdot c_1 \\
 c_3 &= g_2 \cdot \bar{c}_2 + p_2 \cdot c_2 \\
 c_4 &= g_3 \cdot \bar{c}_3 + p_3 \cdot c_3
 \end{aligned}$$

$$\begin{aligned}
 z_3 &= x_3 \oplus y_3 \oplus c_3 = \overline{x_3 \oplus y_3} \cdot c_3 + (x_3 \oplus y_3) \cdot \bar{c}_3 = \\
 &= \overline{x_3 \oplus y_3} (g_2 \bar{c}_2 + p_2 c_2) + (x_3 \oplus y_3) (g_2 \bar{c}_2 + p_2 c_2) = \\
 &= ((\bar{x_3 \oplus y_3}) g_2 + (x_3 \oplus y_3) \bar{g}_2) \bar{c}_2 + ((\bar{x_3 \oplus y_3}) p_2 + (x_3 \oplus y_3) \bar{p}_2) c_2
 \end{aligned}$$

$$\begin{aligned}
 c_4 &= g_3 \bar{c}_3 + p_3 c_3 = \\
 &= g_3 (g_2 \bar{c}_2 + p_2 c_2) + p_3 (g_2 \bar{c}_2 + p_2 c_2) = \\
 &= (g_3 g_2 + p_3 g_2) \bar{c}_2 + (g_3 p_2 + p_3 p_2) c_2
 \end{aligned}$$

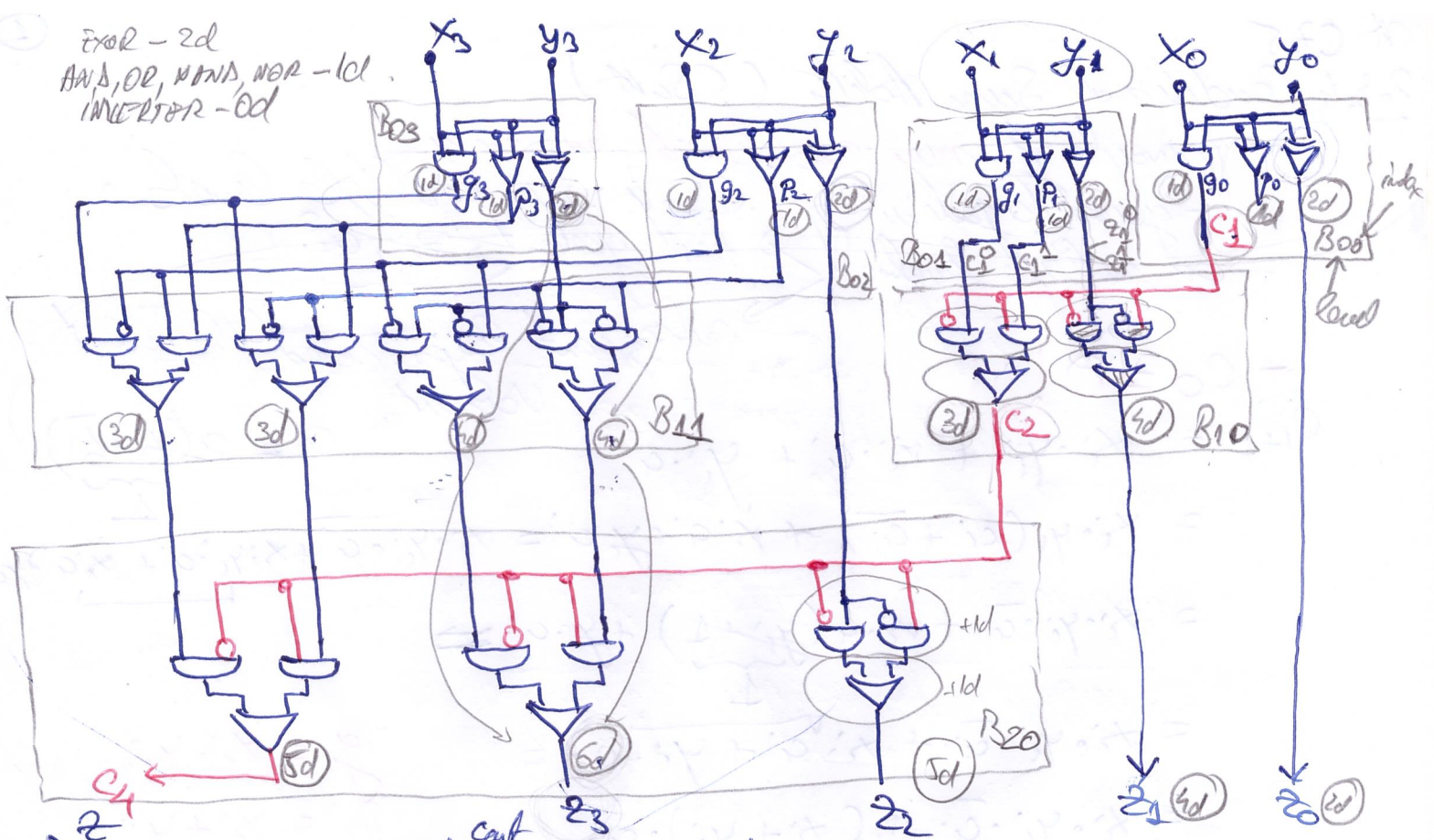
XOR - 2d
 AND, OR, NAND, NOR - 1d
 INVERTER - 0d



$$Des_{out-4} = 6d$$


$$Des_{out-4} = 5d$$

for 2-bit ops

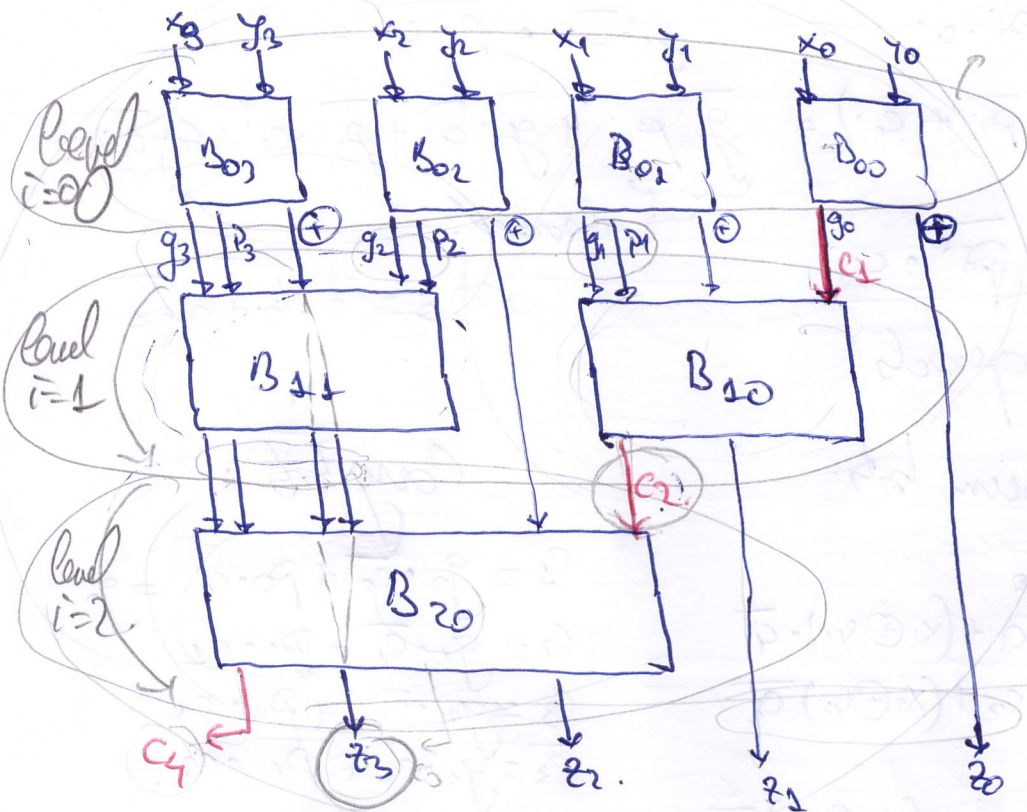

testbook

8-bit CSuA -
block diagram
for 3-bit

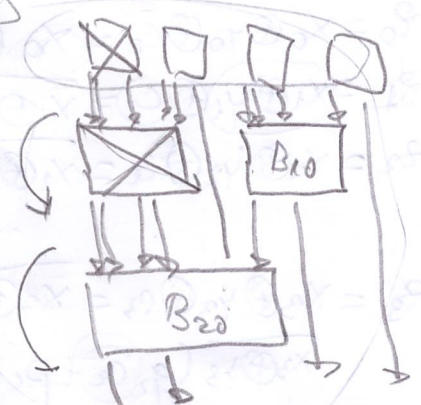

in general: n -bit operands.

$$Des_{out-n} = \underbrace{2d}_{\text{EXOR gate}} + \underbrace{2 \cdot \lceil \log_2 n \rceil d}_{\text{block levels besides the first level}} = 2(\lceil \log_2 n \rceil + 1)d$$

EXOR
gate

block levels
besides the first level

$$\Delta_{CSA}^{cast} = \underbrace{1d}_{g_1 p_1} + 2 \lceil \log_2 n \rceil d = (2 \lceil \log_2 n \rceil + 1) d. \quad (2)$$

Comparison: $n = 64$ bits.

CSA	CSA	HL-CLA	1 CPA
$J^2 = 44d$	$J^2 = (n+2)d = 66d$	$J^2 = (4 \lceil \log_2 n \rceil + 1)d = 25d$	$J^2 = 2nd = 128d$
$J^{cast} = 13d$	$J^{cast} = (n+2)d = 66d$	$J^{cast} = (2 \lceil \log_2 n \rceil + 3)d = 15d$	$J^{cast} = 2nd = 128d$

Example: X, Y - 8-bit.

$$X = 10001101 = 128 + 13 = 141$$

$$Y = 01110101 = 112 + 5 = 117$$

$$C_0 = 0!!!$$

Operand	Rank	7	6	5	4	3	2	1	0
X		1	0	0	0	1	1	0	1
Y		0	1	1	1	0	1	0	1
Block level	Carry in	C	SC	SC	SC	SC	SC	SC	SC
$i=0$	$C_{in}=0$	0	1	0	1	0	1	1	0
	$C_{in}=1$	1	0	1	0	1	0	1	1
$i=1$	$C_{in}=0$	0	1	1	0	1	1	0	0
	$C_{in}=1$	1	0	0	1	0	0	1	1
$i=2$	$C_{in}=0$	0	1	1	1	1	1	0	0
	$C_{in}=1$	1	0	0	0	0	0	1	1
$i=3$	$C_{in}=0$	1	0	0	0	0	0	0	1
	$C_{in}=1$								

Verify:

$$\begin{array}{r}
 \overset{Cast}{1} \quad 1 \quad 0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \quad 1 \\
 0 \quad 1 \quad 1 \quad 1 \quad 0 \quad 1 \quad 0 \quad 1 \\
 \hline
 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 0 \quad 1 \quad 0 = 256 + 2 = 258
 \end{array}$$

$141 + 117 = 258$