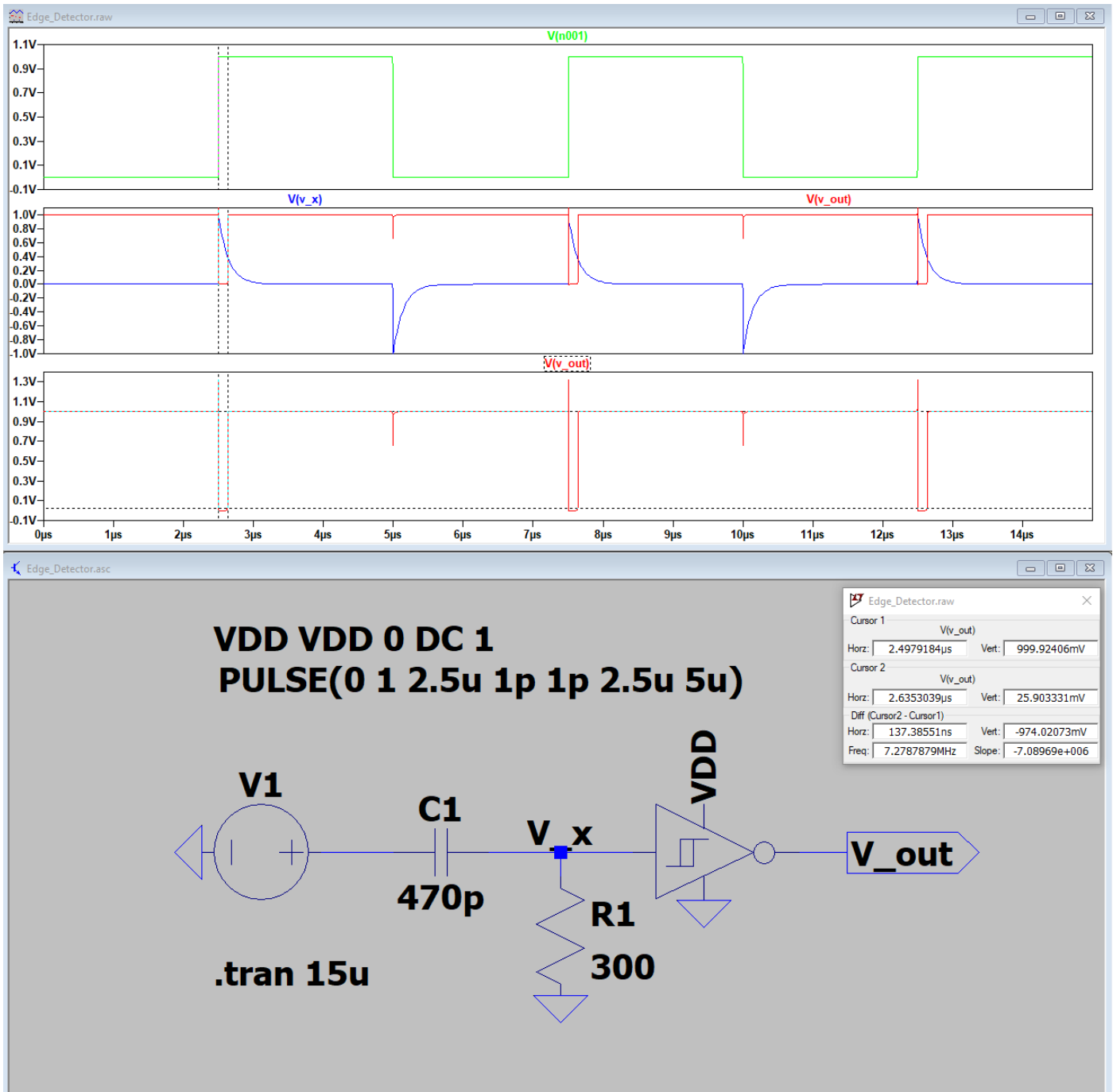


SCHMITT TRIGGER EDGE DETECTOR

Changed the Frequency \rightarrow 200KHz (so some cases will have $T_1 < 2.2RC$)


Changed the Input Voltage Amplitude & VDD \rightarrow 1V (so V_x & V_{out} will drop to 0V, otherwise its about the same)

- $C = 470\text{pF}$ $R = 300\Omega$




Duration of Pulse: 137ns

- $C = 470\text{pF}$ $R = 1000\Omega$

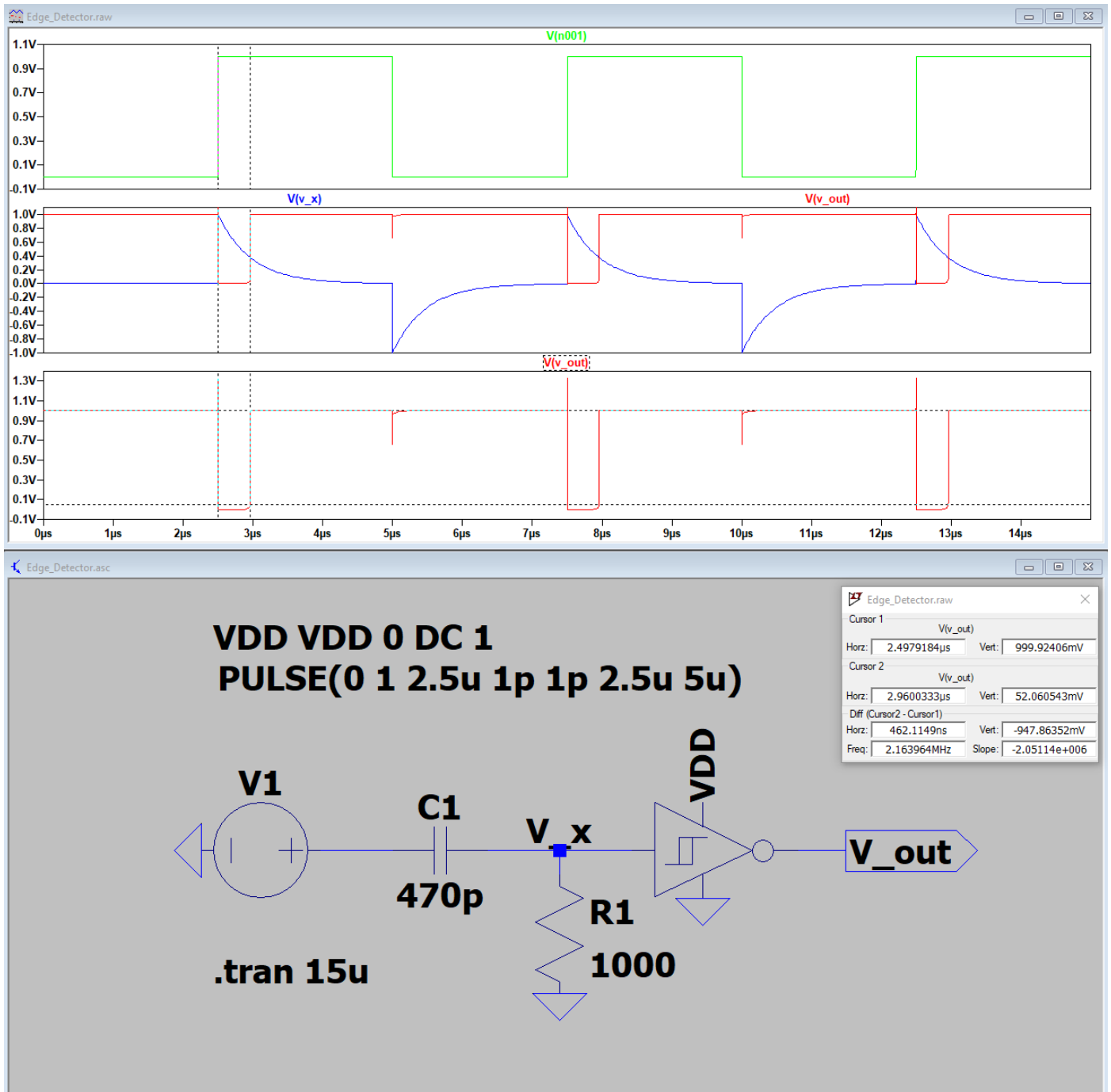


Duration of Pulse: 460ns

- $C = 3.3\text{nF}$ $R = 300\Omega$

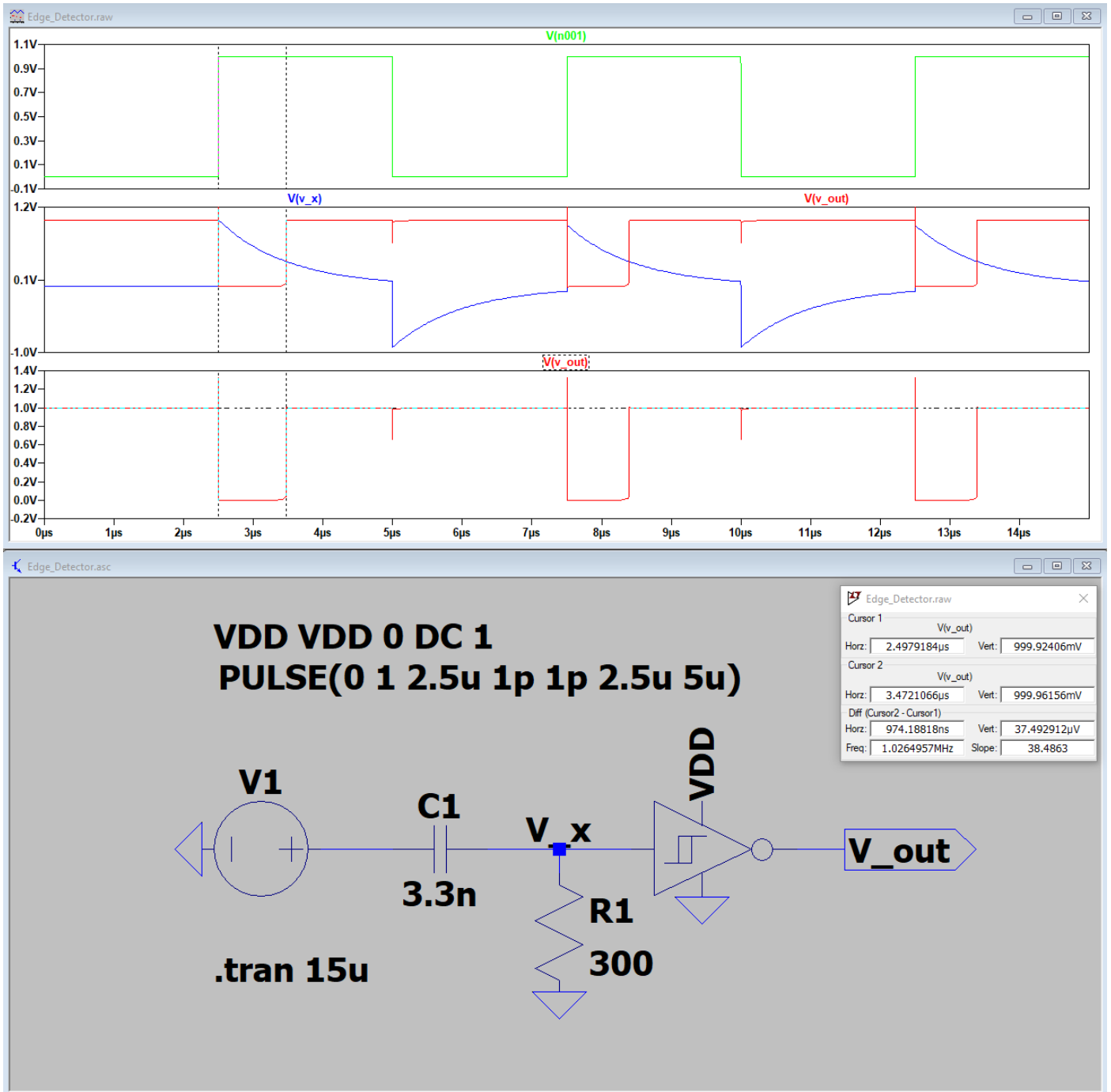


Duration of Pulse: 974ns

- $C = 3.3\text{nF}$ $R = 1000\Omega$

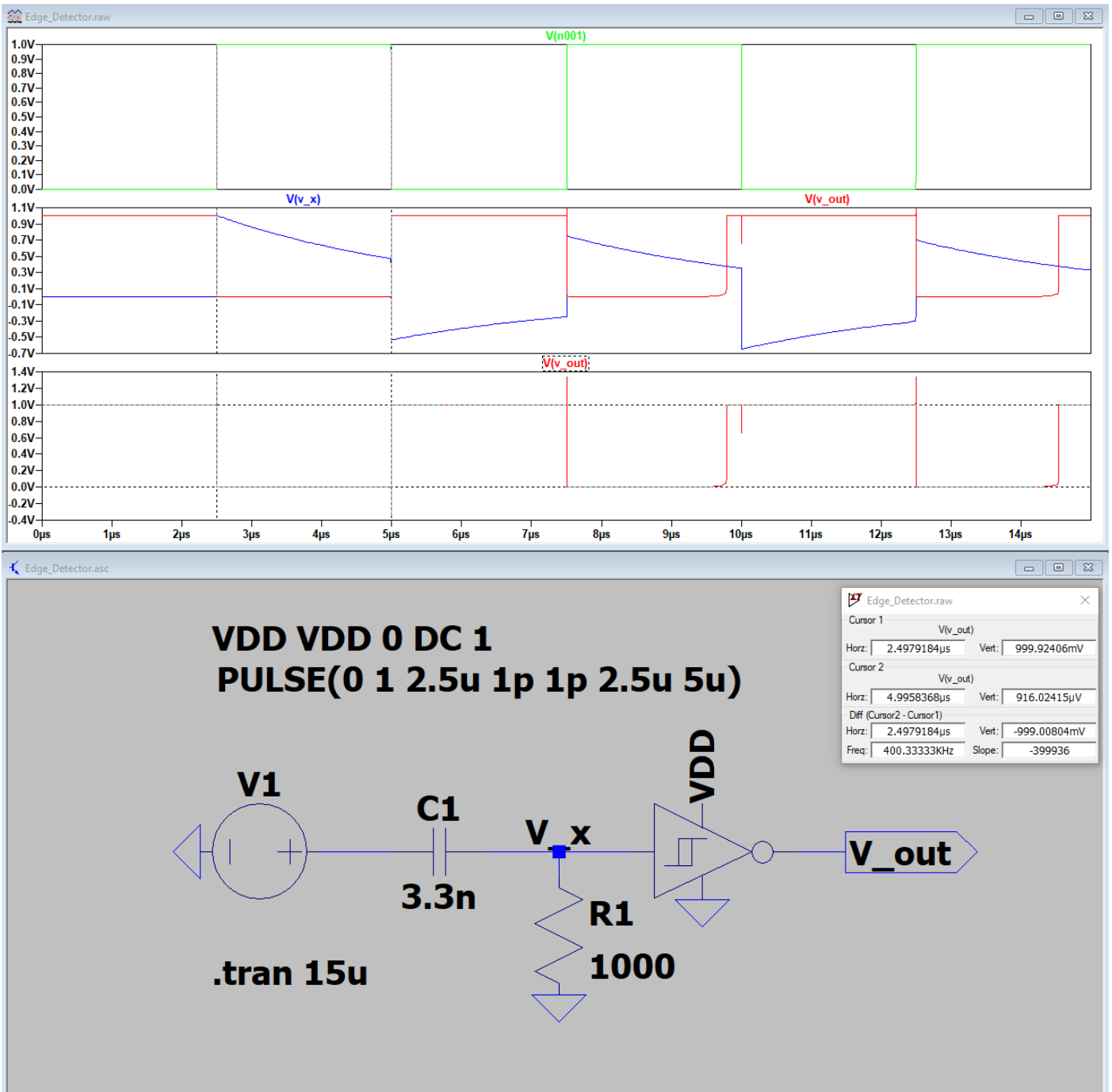


Duration of Pulse: $\approx 2.5\mu\text{s} = T_1$ of Input Voltage, since $T_1 > 2.2RC$

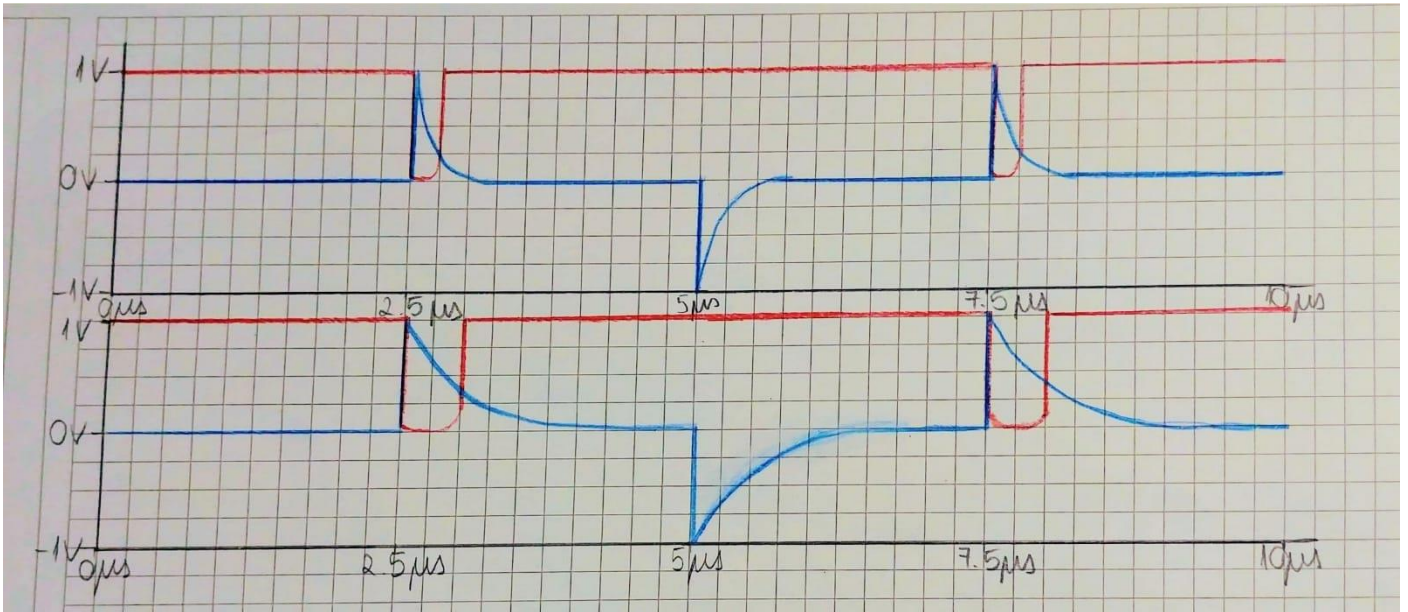- $C = 470\text{pF}$ $R = 300\Omega$
- $C = 470\text{pF}$ $R = 1000\Omega$



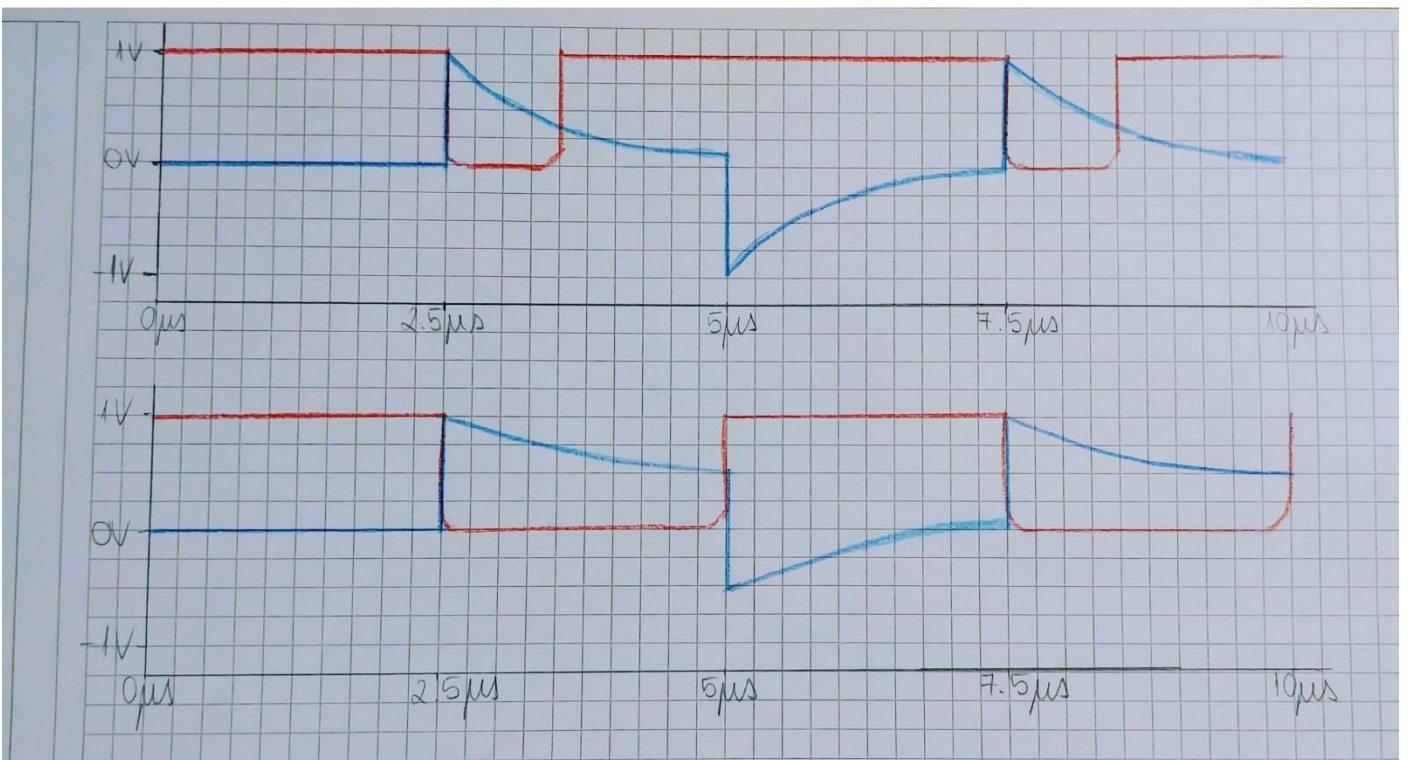- $C = 3.3\text{nF}$ $R = 300\Omega$
- $C = 3.3\text{nF}$ $R = 1000\Omega$



`.include cmosedu_models.txt`

